

國立彰化師範大學 資訊工程學系 硬體描述語言 期中考

2024/11/21

1. Answer the following questions: [24%: (3*8)%]

- (1) What is the “programmable” property of an FPGA chip?
- (2) What is the major purpose for performing “synthesis” for a Verilog-based design?
- (3) In the “inertial delay” model, what kind of input pulse can affect the output of a gate?
- (4) When the delay assumption is made for primitive gates in a design, what is the relation between this delay and the delay of the physical gates after synthesis?
- (5) How to design an adder module that can be used as an 8-bit, 16-bit, or 32-bit adder, etc?
- (6) To show the text messages during simulation, what is the difference between “\$monitor()” and “\$display()”?
- (7) What is the “edge-triggered” property of a D-flipflop?
- (8) In the C/C++ programming, the final product is an executable file, what is the final product of a Verilog-based design?

2. For the Verilog module in Fig. 1, draw its gate-level implementation. [12%]

```
module my_design (x, y, z0, z1, z2);
input    [5:0] x, y;
output   z0, z1, z2;
reg      z2;
reg      [5:0] w;

xor(z0,w[0],w[1]);
assign z1=w[2]|w[3];


integer  i;
always @(x or y) begin
  for (i=0; i <= 5; i = i+1) begin
    if (i<=1)
      w[i]=x[i]&y[i];
    else if (i<=3)
      w[i]=(~x[i])|y[i];
    else
      w[i]=x[i]&(~y[i]);
    end
  end

  z2=~(w[4]|w[5]);
end
endmodule
```


Fig. 1

3. Sketch the simulation waveforms of the modules in (a) Fig. 2, (b) Fig.3, (c) Fig. 4, (d) Fig. 5, and (e) Fig. 6, and (f) Fig. 7. (請標示出信號變化之時間點)


(a) Fig. 2 (my_sim) [8%]

 


(b) Fig. 3 (mod_a) [10%]

 


(c) Fig. 4 (mod_b) [12%]

 


(d) Fig. 5 (mod_c) [10%]

 

(e) Fig. 6 (mod_d) [12%]

 

(f) Fig. 7 (dff) [12%]

 


```

module my_sim (a, b, c, x, y);
input  a, b, c;
output x, y;

xor #2 (x, a, b);
and #2 (y, x, c);
endmodule

```

Fig. 2

```

module mod_a;
reg [3:0] a, b, c;

initial begin
    a = 0; b = 0; c = 0;
end

initial begin
    fork
        #10 a = 1;
        #20 b = 2;
    join

    fork
        #10 b = 3;
        #20 c = 4;
    join

    fork
        a = 5;

        fork
            #10 a = 6;
            #10 b = 7;
            #20 c = 8;
        join

        #30 c = 9;
    join

end

initial
    #100 $finish;
endmodule

```

Fig. 3

```

module mod_b;
reg [3:0] a, b, c, d, e, f;

initial begin
    a=0; b=0; c=0;
    d=0; e=0; f=0;
end

initial begin
    #10
    a <= 1;
    b <= 2;
    a = #10 3;
    b = #10 4;
end

initial begin
    #20
    c = 5;
    d = 6;
    c <= #10 7;
    d <= #10 8;
end

initial begin
    #30
    e <= 9;
    f <= 10;
    e = 11;
    f = 12;
end

initial
    #50 $finish;
endmodule

```

Fig. 4

```

module mod_c;
reg clk;
reg [4:0] a, x1, x2, x3, x4, x5;

initial begin
    clk=0; a=0;
    x1=0; x2=0; x3=0; x4=0; x5=0;
end

initial begin
    #12 a=3; #10 a=6; #10 a=9;
    #10 a=12; #10 a=15; #10 a=18;
    #10 a=21;
end

always
    #10 clk=~clk;

initial
    #15 @(posedge clk) x1=a;
initial
    #15 repeat(3)
        @(posedge clk) x2=a;
initial
    #15 x3 = @(posedge clk) a;
initial
    #15 x4 = repeat(3) @(posedge clk) a;
initial
    #15 @(posedge clk) @(negedge clk) x5=a;

initial
    #100 $finish;
endmodule

```

Fig. 5

a → b → c → d

```

module mod_d;
reg [3:0] a, b, c, d;

initial begin
    a=1; b=2; c=3; d=4;
end

initial begin
    #10
    d <= c; c <= b; b <= a; a <= 5;
end

initial begin
    #20
    d = c; c = b; b = a; a = 6;
end

initial begin
    #30
    a <= 7; b <= a; c <= b; d <= c;
end

initial begin
    #40
    a = 8; b = a; c = b; d = c;
end

initial
    #50 $finish;
endmodule

```

Fig. 6

```

module dff_dlatch(clk, rst, d, y1, y2, y3, y4);
input    clk, rst;
input    [3:0] d;
output   [3:0] y1, y2, y3, y4;
reg      [3:0] y1, y2, y3, y4;

always @(posedge clk or posedge rst)
    y1 = (rst==1) ? 0 : d;

always @(posedge clk)
    y2 = (rst==1) ? 0 : d;

always @(clk or d)
    if (clk==1) y3=d; else y3=y3;

always @(clk or d)
    if (clk==0) y4=d; else y4=4'hz;
endmodule

```

Fig. 7

+12

1. (1) 電路行為可用程式改變

+1 (2) 將程式合成電路

(3) 輸入訊號的持續時間大於 inertial delay

+1 (4) 模擬電路無 delay 或自己加上固定 delay, 實際電路 physical gates 的 delay 會根據晶片大小溫度等因素浮動。

(5)

+1 (6) "\$monitor()" 在所有動作之後才執行輸出, "<=" 之後


"\$display()" 依由上至下的順序執行輸出




(7) D-flip-flop: 當 clk 做正緣/負緣改變的瞬間才可以儲存訊息。

(8)

2


+12

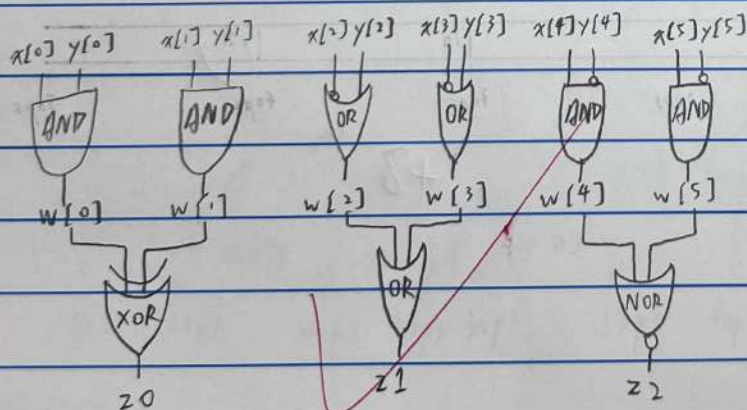

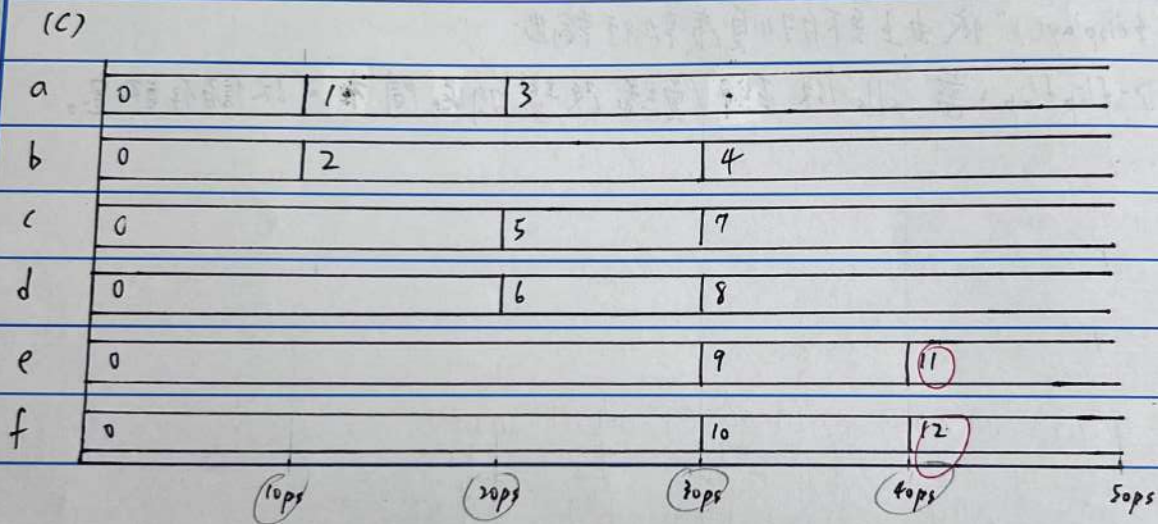  


+8

(d)

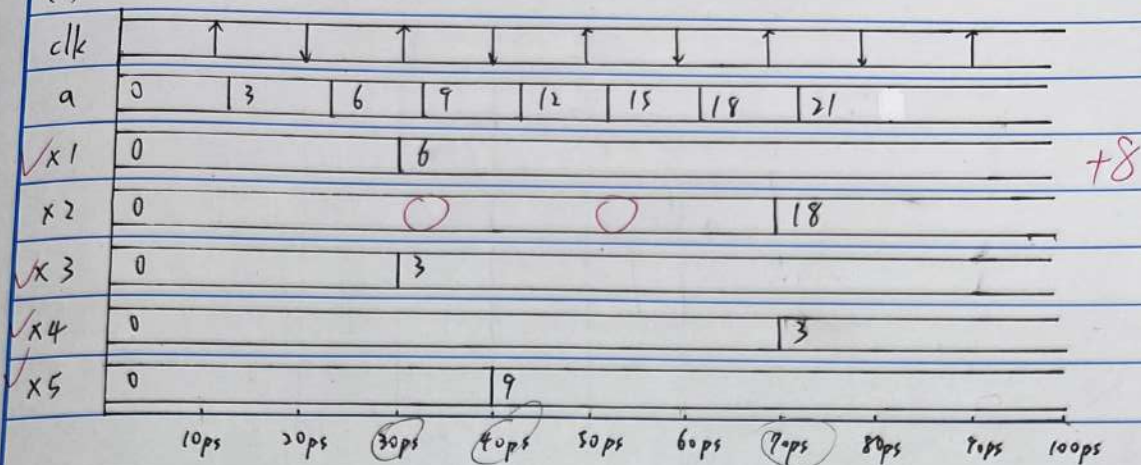

(e)

 

(f)

+12

