

國立彰化師範大學 資訊工程學系 硬體描述語言 期末考

2025/01/09

1. Answer the following questions. [40%: (4*10)%]

- The use of a “reg” variable in Verilog does not imply that the associated behavior is sequential, why?
- What is the difference between a D-type “latch” and a D-type “flip-flop”?
- What is the difference between a signal that is the output of a combinational logic and a signal that is a registered output?
- What is the difference between a Moore machine and a Mealy machine?
- For the one-stage sequential circuit in Fig. 1, what is the constraint of the clock period when data is to be sent correctly from the left flip-flop to the right one?
- For a D-FF, explain the meanings its “setup time” and “hold time”.
- For a Verilog-based design, what is the difference between “function” and “task”?
- For a combinational sorting circuit, how to redesign it to be an 8-stage pipeline?
- Explain the meaning of a “ripple counter”.
- For an incompletely specified “case” statement, a “default” statement, e.g., “default: alu_reg=4'b0;” or “default: alu_reg=4'bx;”, can both be used to make it completely specified, what is the difference between these two statements after the circuit has been synthesized?

 


Fig. 1

2. For the circuit in Fig. 2, use “if...else” statement to complete the Verilog code in Fig. 3. [10%]

 


Fig. 2

*if (sel[0] == 0) {
out = a;
else
out = b;*

```
module mod_a(clk, sel, a, b, c, out);
    input    clk;
    input    [1:0] sel;
    input    [3:0] a, b, c;
    output   [3:0] out;

    // your code here


endmodule
```

Fig. 3

@analysis (

3. For the Verilog description in Fig. 4, sketch the simulation waveforms of signals y1, y2, and y3 (in decimal).

[10%]

 

```

module mod_b (a, b, y1, y2, y3);
input      [3:0] a, b;
output reg [7:0] y1, y2, y3;

always @(a or b)
    y1=(a[1]==1) ? (a+b):(a-b);


always @(a[0] or b[0])
    y2=(b[1]==1) ? (a+b):(a-b);

always @(b[2:1])
    y3=(b[0]==1) ? (a+b):(a-b);
endmodule

```

Fig. 4

 4. For the Verilog description in Fig. 5. (a) Sketch the simulation waveforms of signals sig_a, sig_b, sig_c, and sig_d (in decimal). (b) Draw the schematic design for these four signals. [20%: (12+8)%]




```

module shifter_3 (clk, rst, data_in, sig_a, sig_b, sig_c, sig_d);
input clk, rst;
input [7:0] data_in;
output [7:0] sig_a, sig_b, sig_c, sig_d;


reg [7:0] sig_a, sig_b, sig_c, sig_d;

always @(posedge clk or posedge rst) begin
    if (rst==1) begin
        sig_a=0; sig_b=0; sig_c=0; sig_d=0;
    end
    else begin
        sig_a <= data_in;
        sig_b <= sig_a;
        sig_c <= sig_b+sig_a;
        sig_d <= sig_c+sig_d;
    end
end
endmodule

```

 

 5. The code segment in Fig. 6 is the design of a Mealy machine with registered output. (a) Draw its corresponding state diagram. (b) Sketch the simulation waveforms of signals CS_out and $data_out$. [20%: (10+10)%]



```

module fsm(clk, rst, data_in, CS_out, data_out);
    input  clk, rst, data_in;
    output [1:0] CS_out;
    output [3:0] data_out;
    reg [3:0] data_out;

    reg [1:0] CS, NS; // current state, next state
    assign CS_out=CS;

    reg [3:0] data;

    // state encoding
    parameter s0=2'd0, s1=2'd1, s2=2'd2, s3=2'd3;

    always@(posedge clk or posedge rst) begin
        if (rst==1) begin
            CS=s0; data_out=0;
        end
        else begin
            CS=NS; data_out=data;
        end
    end

    // determine NS
    always@(CS or data_in) begin
        case(CS)
            s0: NS=(data_in==1)?s1:s2;
            s1: NS=(data_in==1)?s0:s3;
            s2: NS=(data_in==1)?s1:s3;
            s3: NS=(data_in==1)?s0:s2;
            default: NS=s0;
        endcase
    end

    // determine data_out
    always@(CS or data_in) begin
        case(CS)
            s0: data=(data_in==1)?1:2;
            s1: data=(data_in==1)?3:4;
            s2: data=(data_in==1)?5:6;
            s3: data=(data_in==1)?7:8;
            default: data_out=0;
        endcase
    end
endmodule

```

Fig. 6

