

硬體描述語言

Chapter 04



# Synthesis of Combinational Logic

Ren-Der Chen (陳仁德)

Department of Computer Science and  
Information Engineering

National Changhua University of Education

E-mail: [rdchen@cc.ncue.edu.tw](mailto:rdchen@cc.ncue.edu.tw)

Fall, 2024

# HDL-Based Synthesis

---

- HDL-based synthesis provides
  - Alternative to gate-level design
  - Higher level of design abstraction
  - Description of overall architecture
  - Description of functionality
- **Synthesis tools** provide
  - Automated gate-level representation
  - Optimal representation
  - Architectural exploration


# HDL Descriptive Style

---

- HDL source style strongly influences synthesized product.
- Rules for descriptive styles are vendor-specific.
- Clocking rules must be observed for **asynchronous** and **synchronous** sequential behavior.
- **Area-delay** tradeoffs are made within the context of a vendor's tool and available technology.

***Not all algorithms are synthesizable!***


# HDL-Based Design Flow

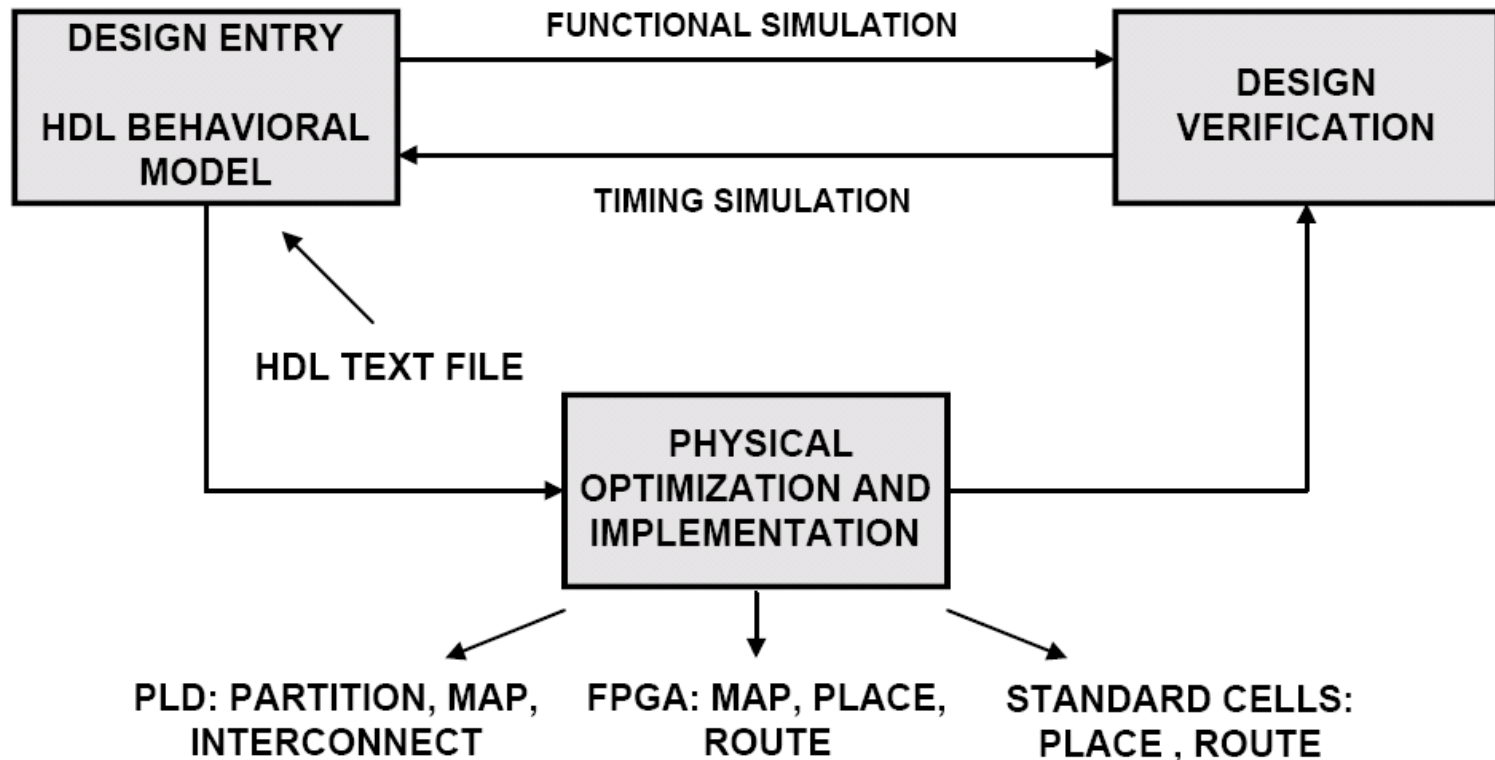

In theory, synthesis tools “**automatically**” create an optimal gate-level realization. In practice, results are dependent upon the skill of the designer using the tool.

# Testbench for Post-Synthesis Design Verification

---

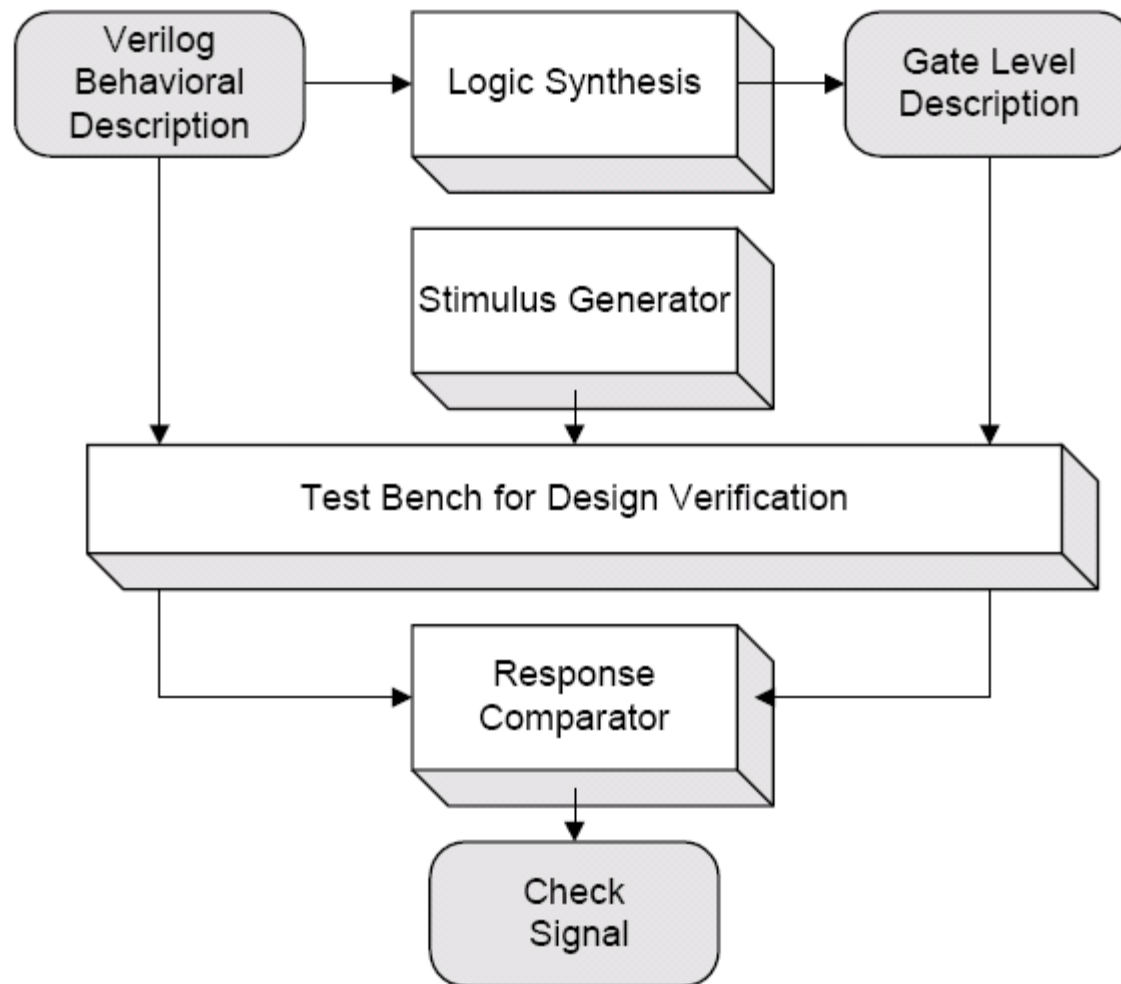

# Levels of Synthesis

---

## ■ Logic synthesis

- Realizes an optimal circuit from a Boolean description.

## ■ RTL synthesis


- Creates a Boolean description from an RTL description.

## ■ Behavioral synthesis

- Creates a RTL description from an algorithmic model of functionality.


# Synthesis Tool Organization

---

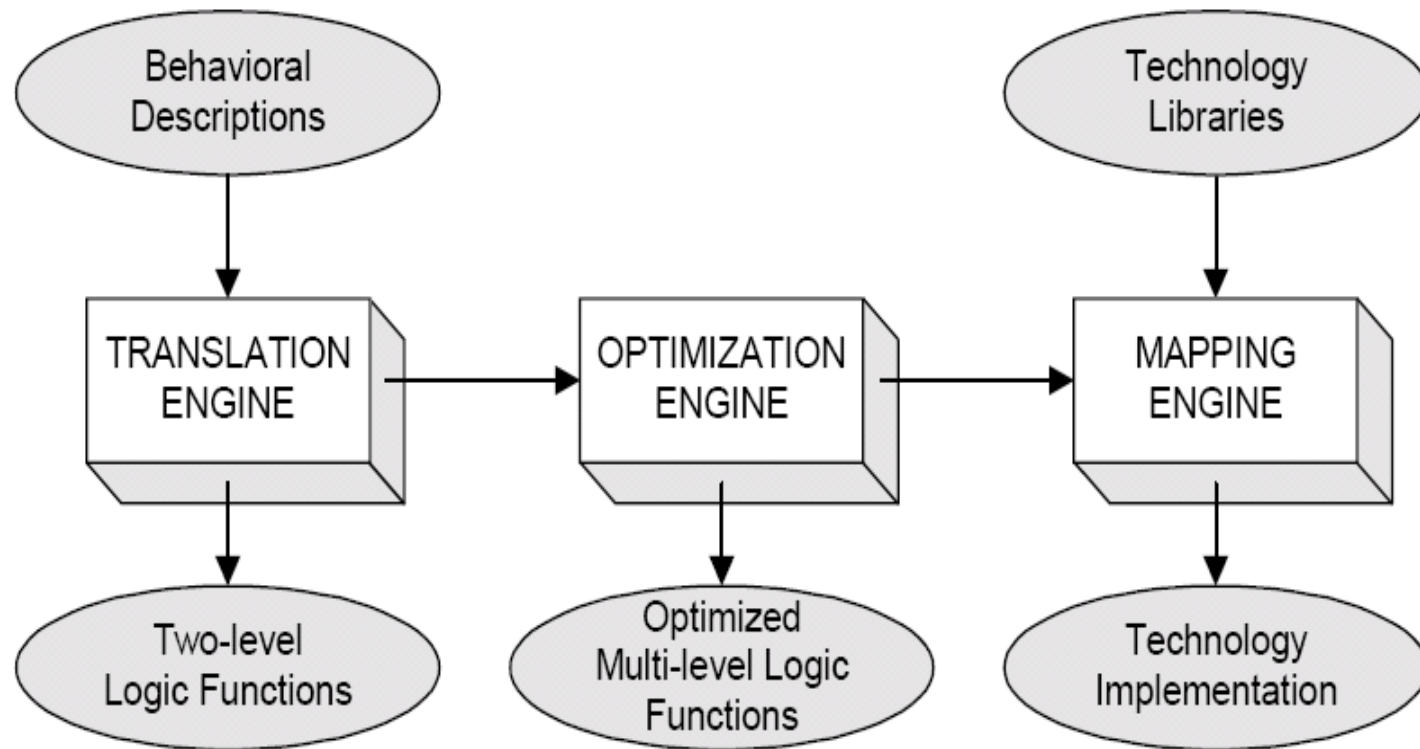

Synthesis of optimal combinational logic is subject to **area**, **speed**, or **power**, etc.

# Multi-Level Combinational Logic

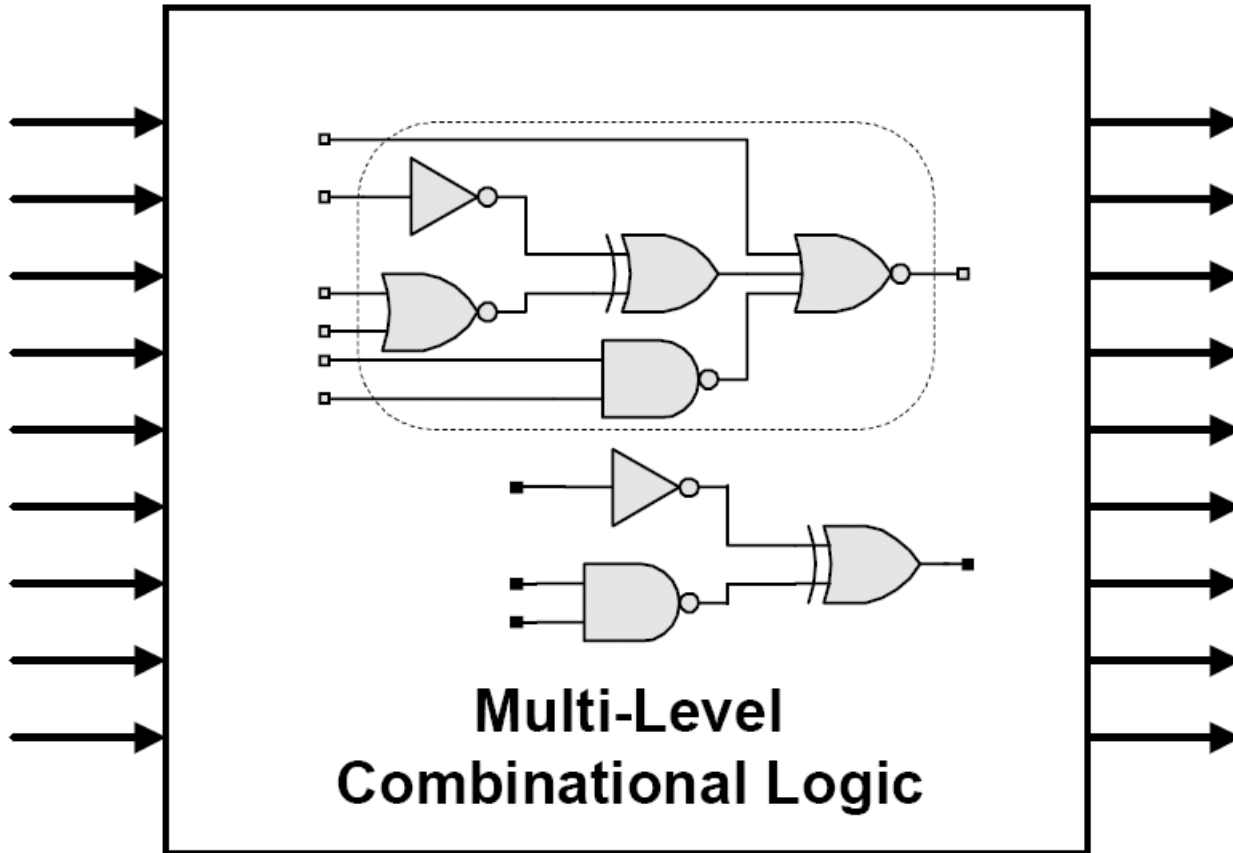

Logic synthesis treats a set of individual Boolean input-output equations as a multi-level circuit.



# Register Transfer Level (RTL) Synthesis

---



- Transforms a behavior described in terms of operations on registers, signals, and constraints.
- Synthesizes an optimal realization in an assumed architecture.
- Begins with the assumptions that a set of hardware resources are available, and that the **scheduling** and **allocation** of resources have been determined by a data-flow graph (DFG).

# Behavioral Synthesis

- Creates an architecture whose resources can be scheduled and allocated to implement an algorithm.

$M = D - A;$   
 $A = B + C;$   
 $D = A * E;$

**Parse trees**

  


**Data-flow graph**
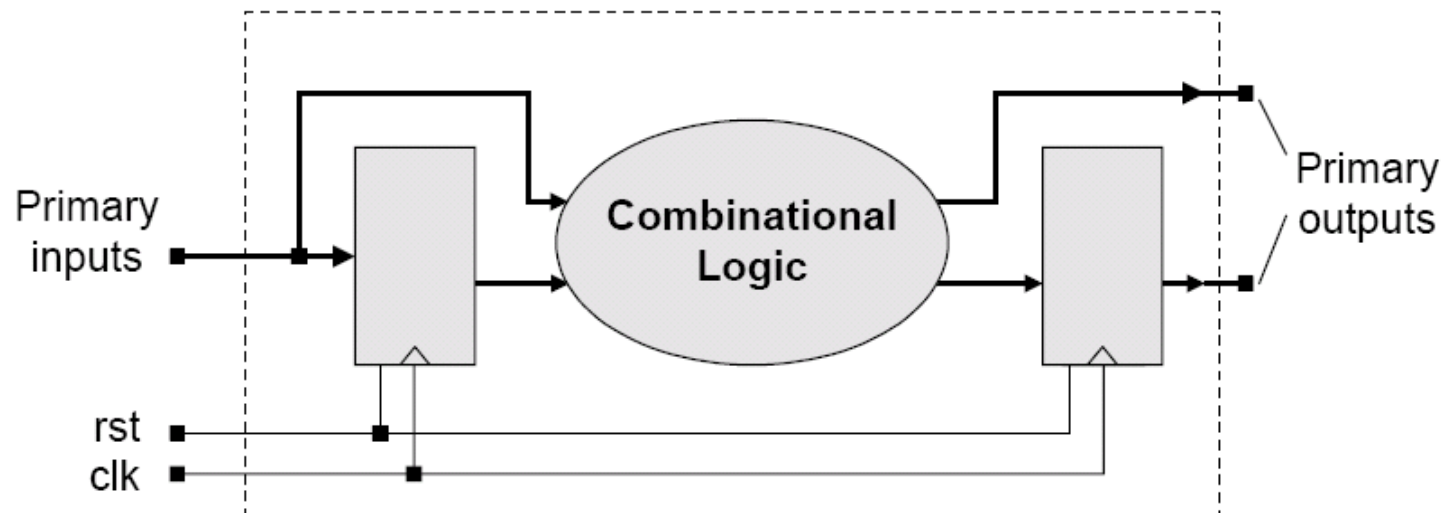
# Structure for Synchronous Logic


---

- Storage elements are triggered by external clock/reset.
- Inputs to combinational logic are primary inputs or are from storage elements.
- The combinational logic is assumed to settle in one clock cycle.


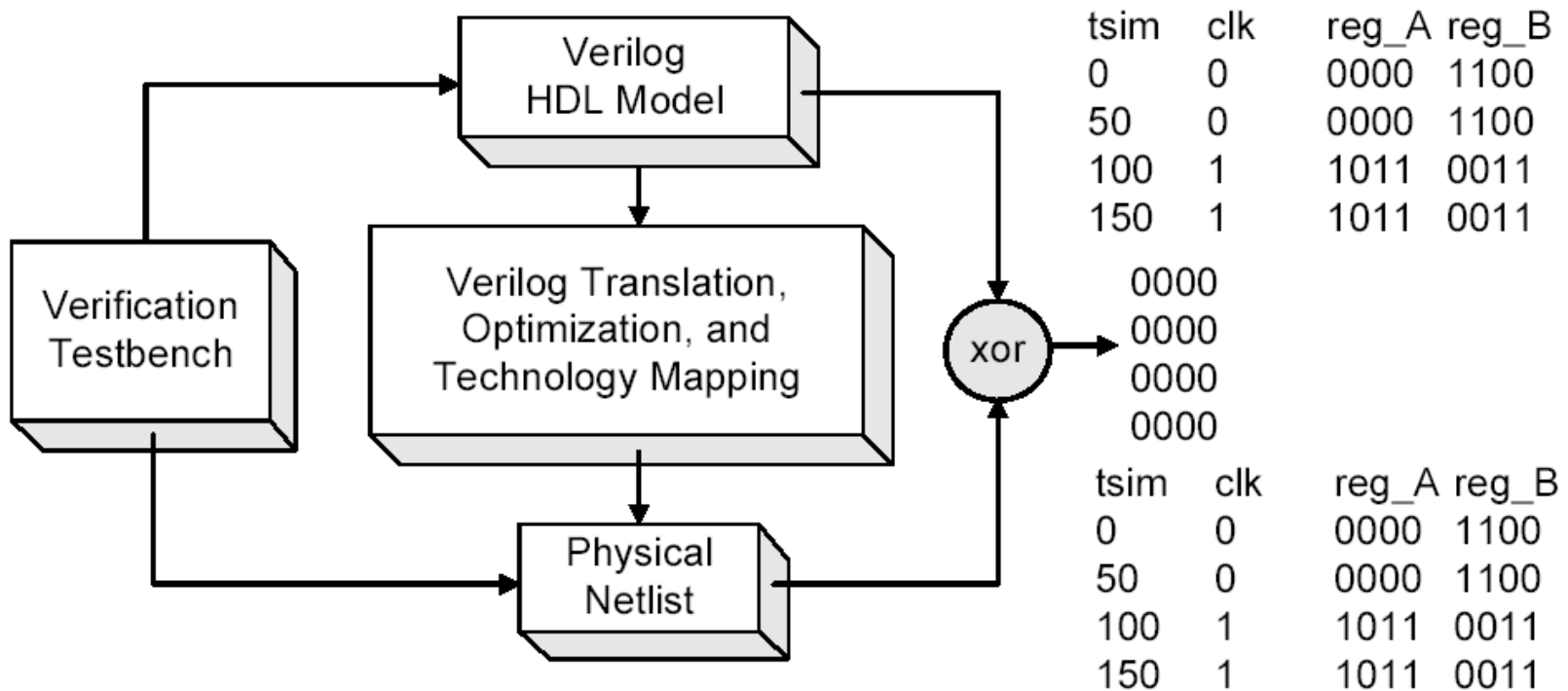
# Match of Pre- and Post-Synthesis Behaviors

- Functionality is independent of delays in the models.
- The outputs of the source description and the synthesized physical netlist must match at the clock edge boundaries.



# Benefits of Synthesis

---

- Fast generation of the gate-level description from the HDL.
- Reduced effort to debug the gate-level design.
- Efficient gate-level implementation.
- Consistency between RTL and gate-level descriptions.
- Technology migration (FPGA, ASIC standard cell).
- Top-down organization with language-based description and documentation.

# Synthesis of Combinational Logic

---

- A Boolean function whose output depends only on the instantaneous **inputs** to the logic, not its **history**.
- No storage elements or memory.

$$\text{Logic\_Output}(t) = f(\text{Logic\_Inputs}(t))$$



# Rules

---

- Avoid technology dependent modeling; i.e. implement **functionality**, not timing.
- The combinational logic *must not have feedback*.
- Specify the output of a combinational behavior for all possible cases of its inputs.
- Logic that is not combinational will be synthesized as **sequential**.

# Combinational Synthesis from a Netlist of Primitives

```
module or_nand_1 (enable, x1, x2, x3, x4, y);
```

```
  input      enable, x1, x2, x3, x4;
```

```
  output     y;
```

```
  wire       w1, w2, w3;
```


```
  or         (w1, x1, x2);
```

```
  or         (w2, x3, x4);
```


```
  or         (w3, x3, x4); // redundant
```

```
  nand       (y, w1, w2, w3, enable);
```

```
endmodule
```

 

Pre-synthesis

 

Post-synthesis

✍ Even if a design is expressed as a netlist of generic primitives, it can still be synthesized to remove any **redundant logic** before mapping into a technology.



# Example 1

```
module boole_opt (a, b, c, d, e, y_out1, y_out2);
```

```
  input      a, b, c, d, e;
```

```
  output     y_out1, y_out2;
```

```
  and (y1, a, c);
```

```
  and (y2, a, d);
```

```
  and (y3, a, e);
```

```
  or  (y4, y1, y2);
```

```
  or  (y_out1, y3, y4);
```

```
  and (y5, b, c);
```



```
  and (y6, b, d);
```

```
  and (y7, b, e);
```


```
  or  (y8, y5, y6);
```

```
  or  (y_out2, y7, y8);
```



```
endmodule
```

 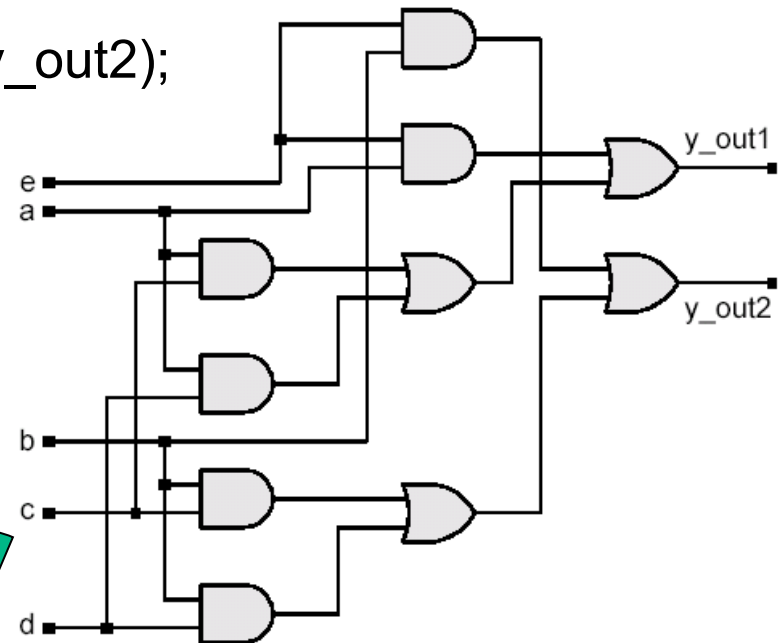

**Logic synthesis**

 

## Example 2

 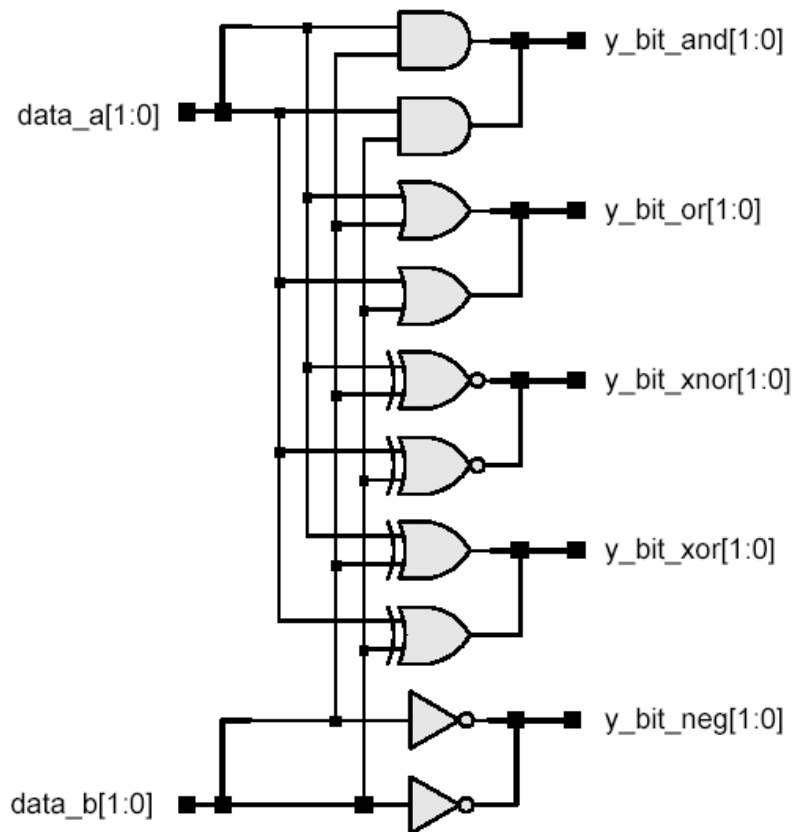


Generic implementation of  
bitwise operations


Synthesized multi-level structure

# Combinational Synthesis from Continuous Assignments

```
module or_nand_2 (enable, x1, x2, x3, x4, y);  
  input          enable, x1, x2, x3, x4;  
  output         y;  
  
  assign         y = ~ (enable & (x1 | x2) & (x3 | x4));  
endmodule
```

 

**Pre-synthesis**

 


**Post-synthesis**
 
# Example

```
module and_gate (a, b, c, y);  
    input        a, b, c;  
    output       y;  
    wire         y1, y2;  
  
    assign       y1 = a & b;  
    assign       y2 = c & b;  
    assign       y  = y1 & y2;  
endmodule
```

- ✍ An **internal net** declared in the source description may be eliminated by the optimization process.
- ✍ A net that is declared as a **primary input or output** will be retained in the synthesized design.



# Combinational Synthesis from a Cyclic Behavior

---

- The behavior must assign value to the output **under all events** that affect the right-hand side expression of the assignment; otherwise, *an unwanted latches will be produced*.
- All inputs to a behavior that is to implement combinational logic must be included in the **event control expression**, either explicitly or implicitly.

# Example 1

```
module or_nand_3 (enable, x1, x2, x3, x4, y);
```

```
  input          enable, x1, x2, x3, x4;
```


```
  output        y;
```

```
  reg          y;
```

```
  always @ (enable or x1 or x2 or x3 or x4)
```

```
    y = ~ (enable & (x1 | x2) & (x3 | x4));
```


```
endmodule
```

 

- ~~✍~~ The use of a **register variable** does **not** imply that the associated behavior is **sequential**.
- ~~✍~~ Nor does it imply that the synthesized hardware will have a **storage** device.
 
## Example 2

```
module n_gate1 (gate_in, y);  
parameter      size = 3;  
input  [size-1: 0] gate_in;  output y;  
reg     y_int;      integer k;  
assign y = y_int;  
always @ (gate_in) begin : look_for_0  
    y_int = 0;  
    for (k=0; k <= size-1; k=k+1)  
        if (gate_in[k] == 0) begin  
            y_int = 1;  
            disable look_for_0;  
        end  
    end  
end  
endmodule
```




- ✍ A **register variable** that is a primary output at the top level of a design will appear in the synthesized result (not necessarily as a storage element).
- ✍ A register variable declared in the source description may be eliminated by the optimization process (e.g., y\_int, k).

## Example 3

---

```
module and4_behav (y, x_in);  
parameter      word_length = 4;  
input  [word_length-1:0] x_in; output y;  
reg      y;  
          integer k;
```

 
```
always @ (x_in) begin: check_for_0  
    y = 1;  
    for (k = 0; k <= word_length -1; k = k+1)  
        if (x_in[k] == 0) begin  
            y = 0;  
            disable check_for_0;  
        end  
    end  
end  
endmodule
```




 
## Example 4

```
module comparator (a, b, a_gt_b, a_lt_b, a_eq_b);  
parameter      size = 2;  
input    [size: 1] a, b;  
output   a_gt_b, a_lt_b, a_eq_b;    reg  a_gt_b, a_lt_b, a_eq_b;  
integer k;  
always @ (a or b) begin: compare_loop  
    for (k = size; k > 0; k = k-1) begin  
        if (a[k] != b[k]) begin  
            a_gt_b = a[k]; a_lt_b = ~a[k]; a_eq_b = 0;  
            disable compare_loop;  
        end  
    end  
    a_gt_b = 0; a_lt_b = 0; a_eq_b = 1;  
end  
endmodule
```




# Combinational Synthesis from a Function

```
module or_nand_4 (enable, x1, x2, x3, x4, y);  
  input          enable, x1, x2, x3, x4;  
  output         y;  
  
  assign         y = or_nand (enable, x1, x2, x3, x4);
```

```
function or_nand;  
  input enable, x1, x2, x3, x4;  
  or_nand = ~ (enable & (x1 | x2) & (x3 | x4));
```

```
endfunction  
endmodule
```

 


# Combinational Synthesis from a Task

```
module or_nand_5 (enable, x1, x2, x3, x4, y);
```

```
  input      enable, x1, x2, x3, x4;
```

```
  output     y;
```

```
  reg        y;
```

 

```
  always @ (enable or x1 or x2 or x3 or x4)
```

```
    or_nand (enable, x1, x2, x3, x4, y);
```

```
task or_nand;
```

```
  input  enable, x1, x2, x3, x4;
```

```
  output y;
```

```
  y = ~ (enable & (x1 | x2) & (x3 | x4));
```

```
endtask
```

```
endmodule
```

# Simulation Efficiency

---

- Use of **procedural-continuous assignment (PCA)** reduces the size of the **event sensitivity list** and improves the **simulation efficiency**.
- **assign** is used without **deassign** to establish a binding between the output and the inputs.
- **deassign** is used only in **sequential** models (e.g., latches), when a previously assigned binding of the register variable is to be released.
- Some tools do not support PCA for synthesis.
- *Two models might be used and switched between simulation and synthesis.*

# Example 1

---

```
module or_nand_6 (enable, x1, x2, x3, x4, y);
```

```
  input          enable, x1, x2, x3, x4;
```

```
  output         y;
```

```
  reg            y;
```

```
  always @ (enable)
```


```
    if (enable)
```

```
      assign y = (x1 | x2) & (x3 | x4);
```

```
    else
```

```
      assign y = 1;
```

```
endmodule
```

 

```
always @ (enable or x1 or x2 or x3 or x4)
```

```
  if (enable)
```

```
    y = (x1 | x2) & (x3 | x4);
```

```
  else
```

```
    y = 1;
```

## Example 2

---

```
always @ (opcode or a or b)
  case (opcode)
    3'b111: out_y = a & b;
    3'b011: out_y = a | b;
    3'b001: out_y = a ^ b;
    default: out_y = 2'bx;
  endcase
```

**Preferred for synthesis**

```
always @ (opcode)
  case (opcode)
    3'b111: assign out_y = a & b;
    3'b011: assign out_y = a | b;
    3'b001: assign out_y = a ^ b;
    default: assign out_y = 2'bx;
  endcase
```

**Preferred for simulation**

# Synthesis of Control Logic for Multiplexed Datapaths

---

// assign / conditional

**module** syn1\_mux\_4bits (a, b, c, d, sel, y);

**input**          [3:0] a, b, c, d;


**input**          [1:0] sel;

**output**        [3:0] y;

**assign** y = (sel == 0) ? a :  
                 (sel == 1) ? b :  
                 (sel == 2) ? c :  
                 (sel == 3) ? d : 4'bx;

**endmodule**
 
# Synthesis Result for “syn1\_mux\_4bits”



Under some specific synthesis tool and technology



# Example 1 多工器

// case / PCA, **may not be synthesized**

```
module syn2_mux_4bits
    (a, b, c, d, sel, y);
input    [3:0] a, b, c, d;
input    [1:0] sel;
output   [3:0] y;
reg     [3:0] y;
```

```
always @((sel)) 決定電路
    case (sel)
        0:    assign y = a; 靜態
        1:    assign y = b;
        2:    assign y = c;
        3:    assign y = d;
        default: assign y = 4'bx;
    endcase
endmodule
```

// **synthesis friendly**

```
module syn2b_mux_4bits
    (a, b, c, d, sel, y);
input    [3:0] a, b, c, d;
input    [1:0] sel;
output   [3:0] y;
reg     [3:0] y;
```

```
always @ (a or b or c or d or sel)
    case (sel)
        0:    y = a;
        1:    y = b;
        2:    y = c;
        3:    y = d;
        default: y = 4'bx;
    endcase
endmodule
```

## Example 2


---

```
// if ... else / PCA,  
// may not be synthesized  
module syn3_mux_4bits  
    (a, b, c, d, sel, y);  
  
input    [3:0] a, b, c, d;  
input    [1:0] sel;  
output   [3:0] y;  
reg      [3:0] y;  
  
always @ (sel)  
    if (sel == 0)      assign y = a;  
    else if (sel == 1) assign y = b;  
    else if (sel == 2) assign y = c;  
    else if (sel == 3) assign y = d;  
    else              assign y = 4'bx;  
  
endmodule
```

```
// synthesis friendly  
module syn3b_mux_4bits  
    (a, b, c, d, sel, y);  
  
input    [3:0] a, b, c, d;  
input    [1:0] sel;  
output   [3:0] y;  
reg      [3:0] y;  
  
always @ (a or b or c or d or sel)  
    if (sel == 0)      y = a;  
    else if (sel == 1) y = b;  
    else if (sel == 2) y = c;  
    else if (sel == 3) y = d;  
    else              y = 4'bx;  
  
endmodule
```

# Synthesis Result for “syn2b\_mux\_4bits” and “syn3b\_mux\_4bits”


---

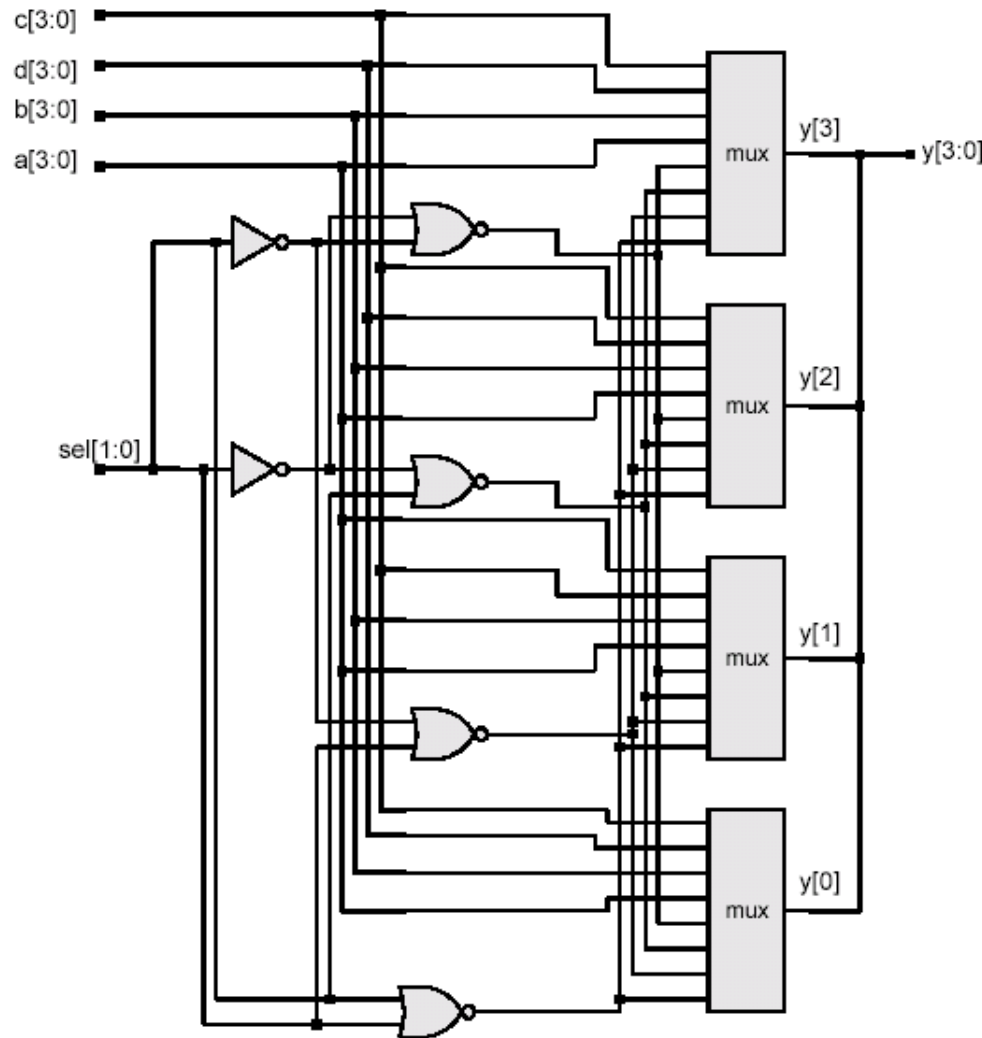

Under some specific synthesis tool and technology

# Synthesis Result for all Three Versions with a Scalar Channel


---

 

# Multiplexer with Selector Logic

---

```
module mux_logic (select, sig_G, sig_max, sig_a, sig_b, y);  
  input select, sig_G, sig_max, sig_a, sig_b;  
  output y;  
  
  assign y = (select == 1) || (sig_G == 1) || (sig_max == 0) ?  
             sig_a : sig_b;  
  
endmodule
```

 

# Unexpected and Unwanted Latches

---


不完全指定

- **Incompletely specified case** statements and conditionals (if statements) may lead to the synthesis of **unwanted latches**.
- When a **case** statement does not specify an output for all possible inputs, the synthesis tool infers an **implicit latch**.
- The description implies that the output should retain its residual value under the conditions that were left unspecified.

# Example

```
module mux_latch (sel_a, sel_b, data_a, data_b, y_out);  
  input      sel_a, sel_b, data_a, data_b;  
  output     y_out;  
  reg        y_out;  
  always @ (sel_a or sel_b or data_a or data_b)  
    case ({sel_a, sel_b})  
      2'b10: y_out = data_a;  
      2'b01: y_out = data_b;  
      // 00, 11: not specified  
    endcase  
endmodule
```

若無指定  
輸出不變 (Latch)

 

# Ex: ALU1

---

```
module alu_incomplete1a (data_a, data_b, enable, opcode, alu_out);
input  [3:0]    data_a, data_b;
input          enable;
input  [2:0]    opcode;
output         alu_out; // Note: scalar, for convenience of illustration
reg  [3:0]     alu_reg;
```

```
assign alu_out = (enable == 1) ? alu_reg : 4'b0;
```

```
always @ (opcodea, b)
    case (opcode)
        3'b001:    alu_reg = data_a | data_b;
        3'b010:    alu_reg = data_a ^ data_b;
        3'b110:    alu_reg = ~data_b;
    endcase
endmodule
```

*error*

Incomplete event control expression and  
**case** statement; no default **case** assignment.



## Ex: ALU2

---

```
module alu_incomplete2a (data_a, data_b, enable, opcode, alu_out);  
input    [3:0]    data_a, data_b;  
input    enable;  
input    [2:0]    opcode;  
output    alu_out; // Note: scalar, for convenience of illustration  
reg      [3:0]    alu_reg;
```

```
assign alu_out = (enable == 1) ? alu_reg : 4'b0;
```

```
always @ (opcode or data_a or data_b) ✓
```

```
    case (opcode)
```

```
        3'b001: alu_reg = data_a | data_b;
```

```
        3'b010: alu_reg = data_a ^ data_b;
```

```
        3'b110: alu_reg = ~data_b;
```


```
    endcase
```

```
endmodule
```

Complete event control expression, but incomplete  
**case** statement; no default **case** assignment.
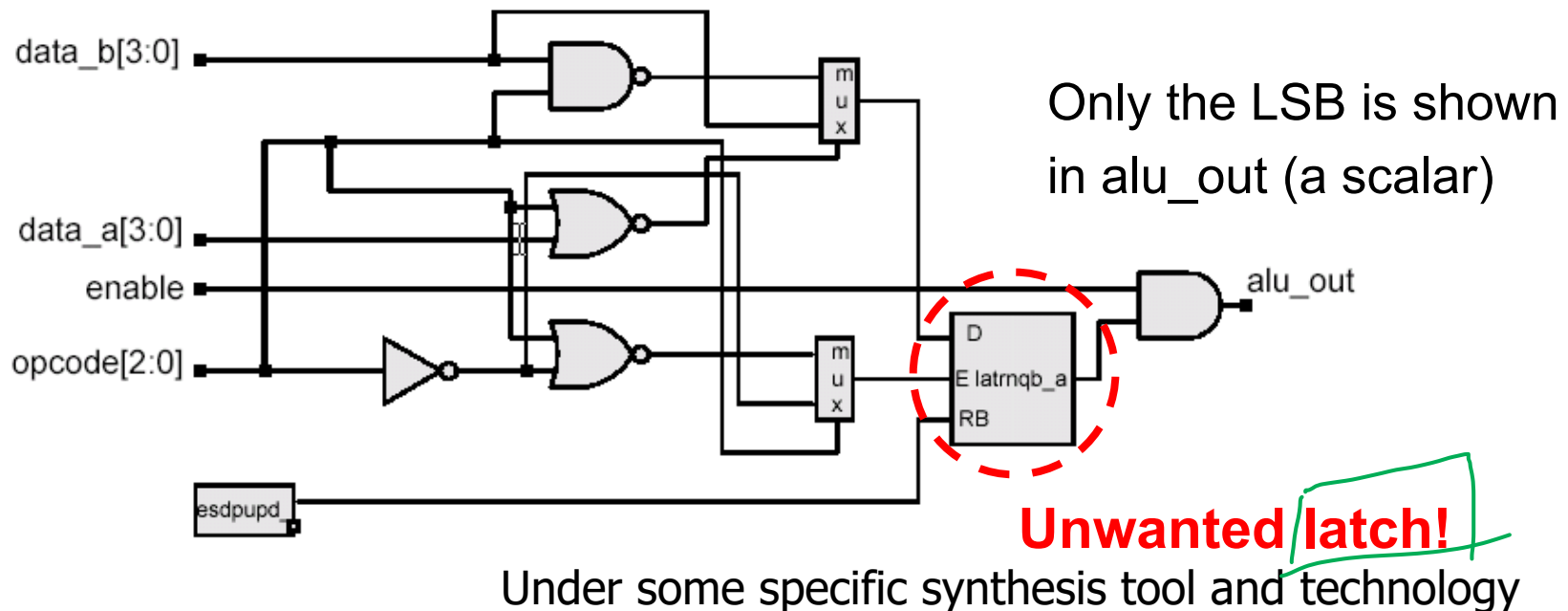
# Synthesis Result for ALU1 & ALU2

- ALU1 and ALU2 synthesize to the same circuit, even though they have different event control expressions.
- They have different pre-synthesis behavior because ALU1 ignores events on the datapath.



## Ex: ALU3

---

```
module alu_complete (data_a, data_b, enable, opcode, alu_out);  
input    [3:0]    data_a, data_b;  
input          enable;  
input    [2:0]    opcode;  
output          alu_out; // Note: scalar, for convenience of illustration  
reg      [3:0]    alu_reg;
```

```
assign alu_out = (enable == 1) ? alu_reg : 4'b0;
```

```
always @ (opcode or data_a or data_b)
```

```
    case (opcode)
```

```
        3'b001:    alu_reg = data_a | data_b;
```

```
        3'b010:    alu_reg = data_a ^ data_b;
```

```
        3'b110:    alu_reg = ~data_b;
```

```
        default:  alu_reg = 4'b0;
```


```
    endcase
```

```
endmodule
```

Complete event control expression  
and default **case** assignment.

# Synthesis Result for ALU3

---

 

**Fully combinational !**

# Alternative Description for ALU3

---

```
module alu_complete2 (data_a, data_b, enable, opcode, alu_out);  
input    [3:0]    data_a, data_b;  
input          enable;  
input    [2:0]    opcode;  
output          alu_out; // Note: scalar, for convenience of illustration  
reg      [3:0]    alu_reg;
```

```
assign alu_out = (enable == 1) ? alu_reg : 4'b0;  
always @ (opcode)  
    case (opcode)  
        3'b001: assign alu_reg = data_a | data_b;  
        3'b010: assign alu_reg = data_a ^ data_b;  
        3'b110: assign alu_reg = ~data_b;  
        default: assign alu_reg = 4'b0;
```

```
    endcase  
endmodule
```

Complete event control expression  
and default **case** assignment.

## Ex: ALU4

---

```
module alu_z1 (data_a, data_b, enable, opcode, alu_out);
input  [3:0]    data_a, data_b;
input          enable;
input  [2:0]    opcode;
output         alu_out; // Note: scalar, for convenience of illustration
reg  [3:0]     alu_reg;
```

```
assign alu_out = (enable == 1) ? alu_reg : 4'bz;
```

高阻态 → bus

```
always @ (opcode or data_a or data_b)
  case (opcode)
    3'b001: alu_reg = data_a | data_b;
    3'b010: alu_reg = data_a ^ data_b;
    3'b110: alu_reg = ~data_b;
    default: alu_reg = 4'b0;
```

```
  endcase
endmodule
```

## Ex: ALU5

```
module alu_z2 (data_a, data_b, enable, opcode, alu_out);  
input  [3:0]    data_a, data_b;  
input          enable;  
input  [2:0]    opcode;  
output         alu_out; // Note: scalar, for convenience of illustration  
reg  [3:0]      alu_reg;
```

```
assign alu_out = (enable == 1) ? alu_reg: 4'bz;
```

```
always @ (opcode or data_a or data_b)
```

```
case (opcode)
```

```
    3'b001:    alu_reg = data_a | data_b;
```

```
    3'b010:    alu_reg = data_a ^ data_b;
```

```
    3'b110:    alu_reg = ~data_b;
```


```
    default:    alu_reg = 4'bx;
```

```
endcase
```

```
endmodule
```

若用不到可設為X  
更易化簡→面積更小

# Synthesis Results

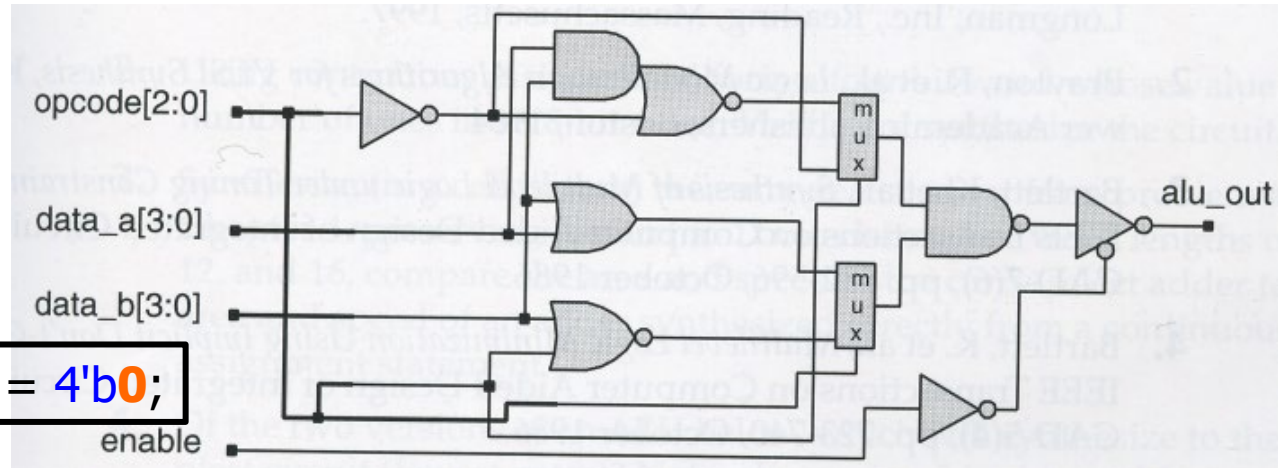


**default:** alu\_reg = 4'b0;

**alu\_z1**

**assign** alu\_out = (enable == 1) ? alu\_reg : 4'bz;

**default:** alu\_reg = 4'bx;

 

**alu\_z2**



# Example

```
module incomplete_and (a1, a2, y);
```

```
input  a1, a2;
```

```
output y;
```

```
reg    y;
```

```
always @ (a1 or a2) begin
```


```
    if ({a2, a1} == 2'b11) y = 1; else
```

```
    if ({a2, a1} == 2'b01) y = 0; else
```

```
    if ({a2, a1} == 2'b10) y = 0;
```

```
end
```

```
endmodule
```

 

# Synthesis of Priority Structures

---

- A **case** statement implicitly attaches **higher priority** to the **first** case\_item than to the last one.
- An **if** statement implies higher priority to the **first** branch than to the remaining branches.
- A synthesis tool will determine whether or not the case items of a **case** statement are **mutually exclusive**.
- If they are, the synthesis tool will treat them as though they had equal priority and will synthesize a **mux** rather than **priority structure**.

# Example

---

```
module mux_4pri (a, b, c, d, sel_a, sel_b, sel_c, y);
```

```
  input      a, b, c, d, sel_a, sel_b, sel_c;
```

```
  output     y;
```

```
  reg        y;
```

```
  always @ (a or b or c or d or sel_a or sel_b or sel_c) begin
```


```
    if (sel_a == 1) y = a; else
```

```
    if (sel_b == 0) y = b; else
```

```
    if (sel_c == 1) y = c; else  
        y = d;
```

```
  end
```

```
endmodule
```

 

# Treatment of Default Conditions

```
module encoder (Data, Code);  
    input      [7:0]    Data;  
    output     [2:0]    Code;  
    reg [2:0]    Code;  
    always @ (Data)  
        if (Data == 8'b00000001) Code = 0; else  
        if (Data == 8'b00000010) Code = 1; else  
        if (Data == 8'b00000100) Code = 2; else  
        if (Data == 8'b00001000) Code = 3; else  
        if (Data == 8'b00010000) Code = 4; else  
        if (Data == 8'b00100000) Code = 5; else  
        if (Data == 8'b01000000) Code = 6; else  
        if (Data == 8'b10000000) Code = 7; else  
                                Code = 3'bx;
```



```
always @ (Data)  
    case (Data)  
        8'b00000001 : Code = 0;  
        8'b00000010 : Code = 1;  
        8'b00000100 : Code = 2;  
        8'b00001000 : Code = 3;  
        8'b00010000 : Code = 4;  
        8'b00100000 : Code = 5;  
        8'b01000000 : Code = 6;  
        8'b10000000 : Code = 7;  
        default: Code = 3'bx;  
    endcase
```

```
endmodule
```

The default assignment is necessary to prevent synthesis of a latch, and the default condition will be "don't cares" in synthesis.

# Synthesis Result

---

  

## 8:3 Priority Encoder 编码

```
module priority (Data, Code, valid_data);
```

```
    input          [7:0]    Data;
```

```
    output         [2:0]    Code;
```

```
    output                    valid_data;
```

```
    reg             [2:0]    Code;
```

```
    assign          valid_data = |Data;
```

```
    always @ (Data)
```

```
        if (Data[7]) Code = 7; else
```

```
        if (Data[6]) Code = 6; else
```

```
        if (Data[5]) Code = 5; else
```

```
        if (Data[4]) Code = 4; else
```

```
        if (Data[3]) Code = 3; else
```

```
        if (Data[2]) Code = 2; else
```

```
        if (Data[1]) Code = 1; else
```

```
        if (Data[0]) Code = 0; else
```

```
            Code = 3'bx;
```

```
endmodule
```

```
always @ (Data)
```

```
    casex (Data)
```

```
        8'b1xxxxxxx : Code = 7;
```

```
        8'b01xxxxxx : Code = 6;
```

```
        8'b001xxxxx : Code = 5;
```

```
        8'b0001xxxx : Code = 4;
```

```
        8'b00001xxx : Code = 3;
```

```
        8'b000001xx : Code = 2;
```


```
        8'b0000001x : Code = 1;
```

```
        8'b00000001 : Code = 0;
```

```
        default:      Code = 3'bx;
```

```
    endcase
```

# Synthesis Result

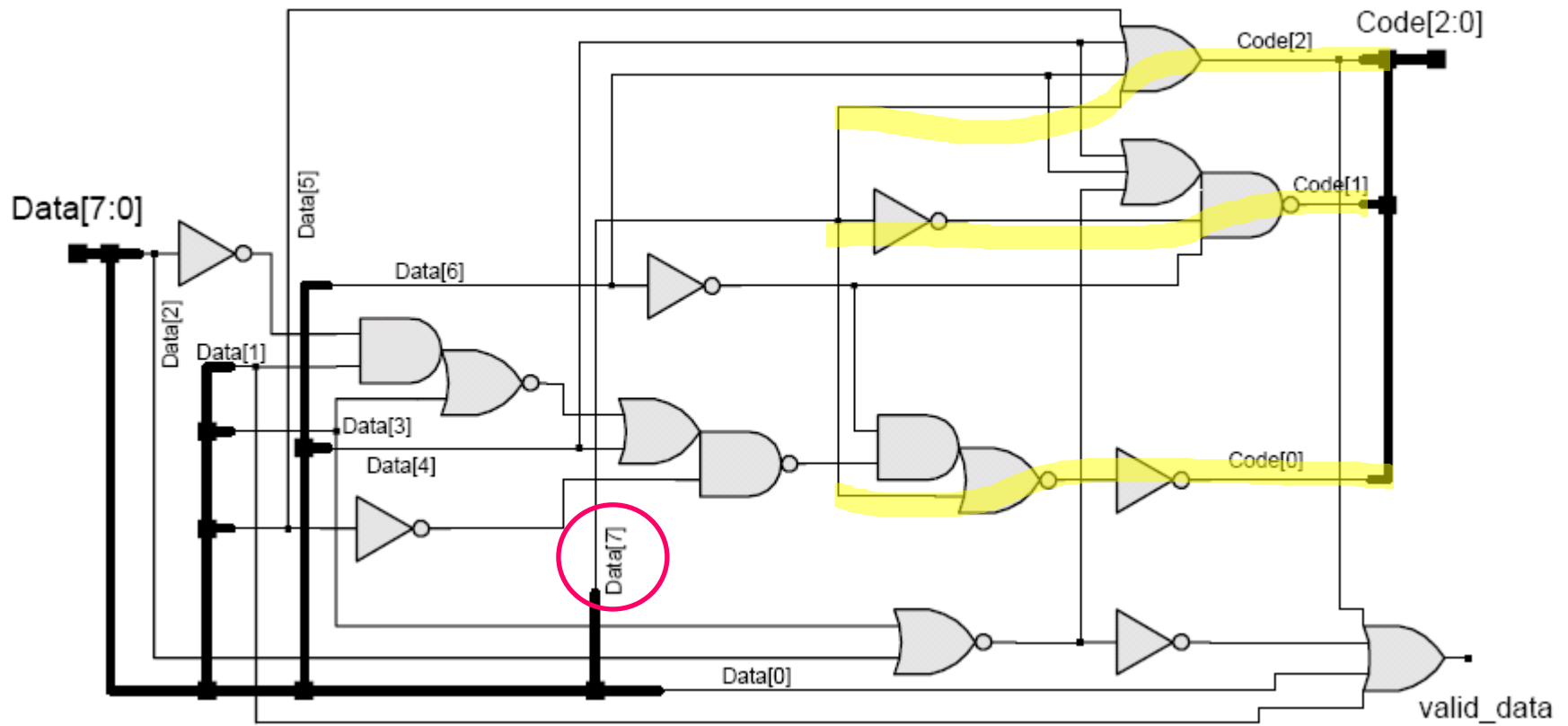


## 3:8 Decoder

解碼


```
module decoder (Code, Data);  
    input      [2:0]    Code;  
    output     [7:0]    Data;  
    reg        [7:0]    Data;  
    always @ (Code) begin  
        if (Code == 0) Data = 8'b00000001; else  
        if (Code == 1) Data = 8'b00000010; else  
        if (Code == 2) Data = 8'b00000100; else  
        if (Code == 3) Data = 8'b00001000; else  
        if (Code == 4) Data = 8'b00010000; else  
        if (Code == 5) Data = 8'b00100000; else  
        if (Code == 6) Data = 8'b01000000; else  
        if (Code == 7) Data = 8'b10000000; else  
            Data = 8'bx;  
    end  
endmodule
```
 
```
always @ (Code)  
    case (Code)  
        0 : Data = 8'b00000001;  
        1 : Data = 8'b00000010;  
        2 : Data = 8'b00000100;  
        3 : Data = 8'b00001000;  
        4 : Data = 8'b00010000;  
        5 : Data = 8'b00100000;  
        6 : Data = 8'b01000000;  
        7 : Data = 8'b10000000;  
        default: Data = 8'bx;  
    endcase
```






# Synthesis Result

 

# Combinational 7-Segment Display

 

```

module sev_seg_display (data_in, data_out);
    input      [3:0]    data_in;
    output     [6:0]    data_out;
    reg        [6:0]    data_out;
    // active low output, abc_defg
    parameter BLNK      = 7'b111_1111;
    parameter ZERO      = 7'b000_0001;
    parameter ONE       = 7'b100_1111;
    parameter TWO       = 7'b001_0010;
    parameter THREE     = 7'b000_0110;
    parameter FOUR      = 7'b100_1100;
    parameter FIVE      = 7'b010_0100;
    parameter SIX       = 7'b010_0000;
    parameter SEVEN     = 7'b000_1111;
    parameter EIGHT     = 7'b000_0000;
    parameter NINE      = 7'b000_0100;

    always @ (data_in)
        case (data_in)
            0: data_out = ZERO;
            1: data_out = ONE;
            2: data_out = TWO;
            3: data_out = THREE;
            4: data_out = FOUR;
            5: data_out = FIVE;
            6: data_out = SIX;
            7: data_out = SEVEN;
            8: data_out = EIGHT;
            9: data_out = NINE;
            default: data_out = BLNK;
        endcase
    endmodule
    
```

# Latched 7-Segment Display (1/2)


---

```
module latched_sev_seg_display
(blanking, enable, clock, reset, display_L, display_R,);
input          blanking, enable, clock, reset;
output [6: 0]   display_L, display_R; reg [6: 0]   display_L, display_R;
reg          [3: 0]   count;
// active low output
parameter BLNK          = 7'b111_1111;
parameter ZERO          = 7'b000_0001;
parameter ONE           = 7'b100_1111;
parameter TWO           = 7'b001_0010;
parameter THREE         = 7'b000_0110;
parameter FOUR          = 7'b100_1100;
parameter FIVE          = 7'b010_0100;
parameter SIX           = 7'b010_0000;
parameter SEVEN         = 7'b000_1111;
parameter EIGHT         = 7'b000_0000;
parameter NINE          = 7'b000_0100;
```
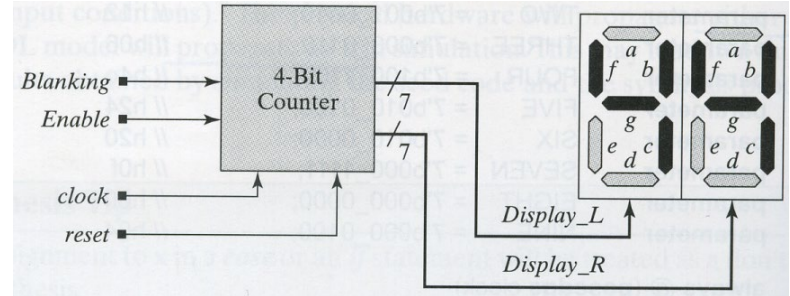
# Latched 7-Segment Display (2/2)

```
always @ (posedge clock)
  if (reset) count <= 0;
  else if (enable) count <= count +1;
always @ (count or blanking)
  if (blanking) begin display_L = BLNK; display_R = BLNK; end else
    case (count)
      0:      begin display_L = ZERO; display_R = ZERO; end
      2:      begin display_L = ZERO; display_R = TWO; end
      4:      begin display_L = ZERO; display_R = FOUR; end
      6:      begin display_L = ZERO; display_R = SIX; end
      8:      begin display_L = ZERO; display_R = EIGHT; end
      10:     begin display_L = ONE; display_R = ZERO; end
      12:     begin display_L = ONE; display_R = TWO; end
      14:     begin display_L = ONE; display_R = FOUR; end
      // default: begin display_L = BLNK; display_R = BLNK; end
    endcase
endmodule
```

The absence of default assignments latches the output and will cause latches to be implemented by a synthesis tool.




# Technology Mapping and Shared Resources

---


```
module badd_4 (a, b, c_in, sum, c_out);  
    input          [3:0]    a, b;  
    input          c_in;  
    output         [3:0]    sum;  
    output         c_out;  
  
    assign         {c_out, sum} = a + b + c_in;  
endmodule
```

Synthesis tools include a **technology mapping engine** that covers the generic, optimized multi-level Boolean description of the circuit by the **physical gates** in a technology library.

# Synthesis Results

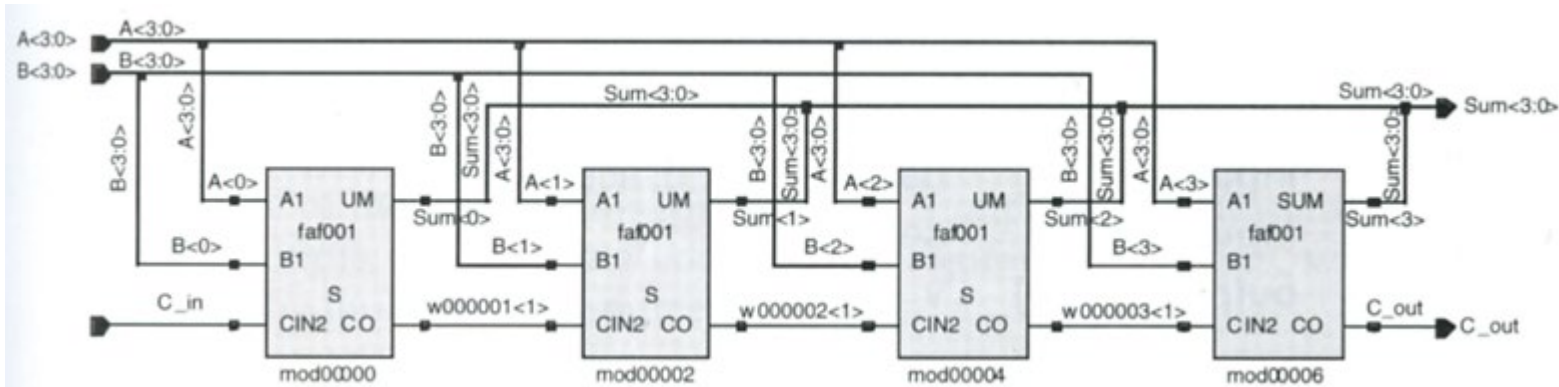

**Using full-adder cells**

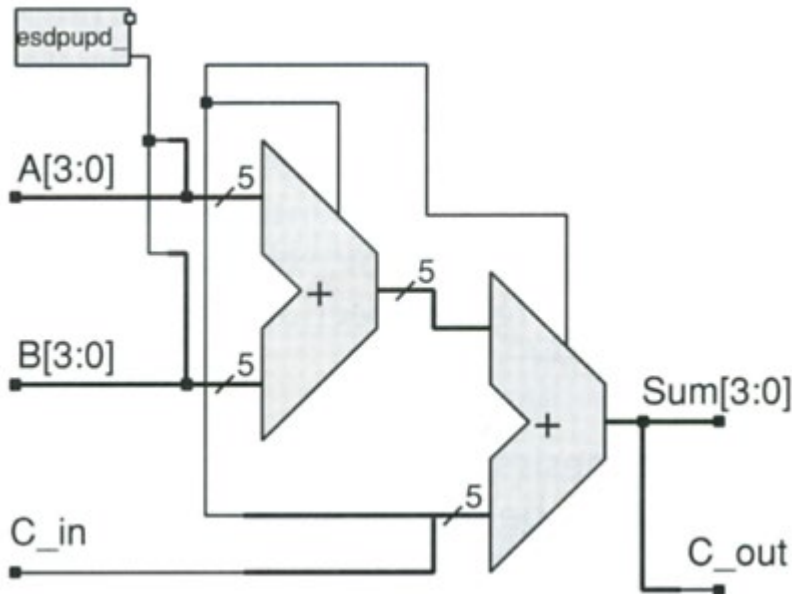


**Using 5-bit adder cells  
depending on the speed goal**

Under some specific synthesis tool and technology
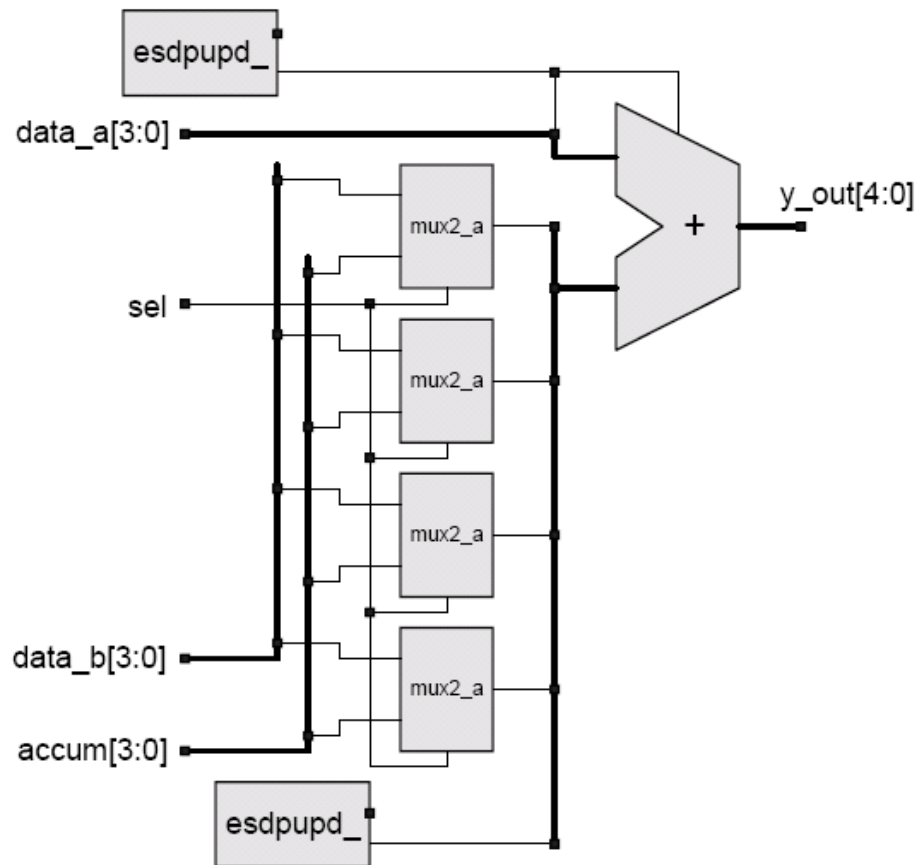
# Example

**assign** y\_out = sel ? data\_a + accum : data\_a + data\_b;

➔ **assign** y\_out = data\_a + (sel ? accum : data\_b);



# Three-State Buffers

---

- **Three-state devices** are controlled by a signal whose value determines whether an input signal is connected to the output.
- This functionality is important in physical circuits having **multiple drivers**, e.g., bus.



# Buses

---

```
module stuff_to_bus1 (bus_enabled, clk, data_to_bus);
```

```
  input                bus_enabled, clk;
```

```
  output      [31:0]  data_to_bus;
```


```
  reg         [31:0]  ckt_output_to_bus;
```

```
  assign data_to_bus = (bus_enabled) ? ckt_output_to_bus : 32'bz;
```

```
  ...
```

```
endmodule
```

Unidirectional interface to a bus

 

The speed at which a bus can operate is limited by the **capacitive loading** placed on it.


# Bi-Directional Bus Drivers

```
module stuff_to_bus2 (clk, send_data, rcv_data, data_to_from_bus);  
    input                clk, send_data, rcv_data;  
    inout                [31:0] data_to_from_bus;  
    reg                  [31:0] reg_to_bus;  
    wire                 [31:0] data_to_from_bus, inbound_data;
```

```
    assign inbound_data = (rcv_data) ? data_to_from_bus : 32'bz;  
    assign data_to_from_bus = (send_data) ? reg_to_bus:  
        data_to_from_bus;
```

...

```
endmodule
```

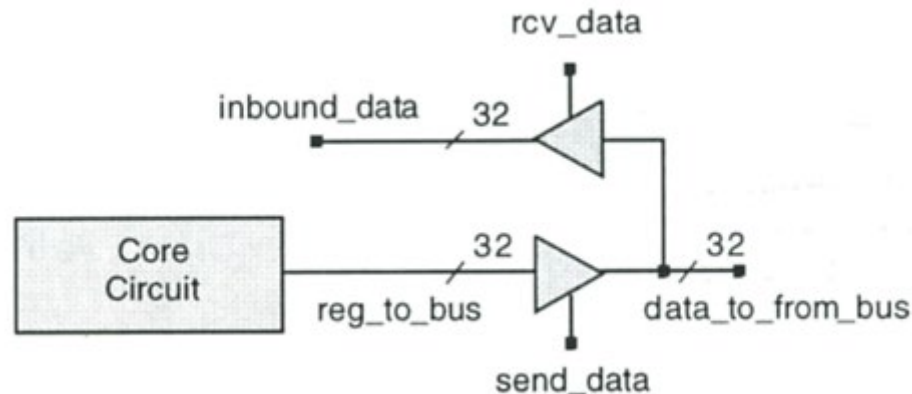

# Multiplexed Bus Drivers

```
module stuff_to_bus3 (enab_a, enab_b, clk, rcv_data,  
    data_to_from_bus);
```

```
    input                enab_a, enab_b, clk, rcv_data;
```


```
    inout    [31:0]    data_to_from_bus;
```

```
    reg      [31:0]    reg_a_to_bus, reg_b_to_bus;
```

```
    assign data_to_from_bus = (enab_a) ? reg_a_to_bus : (enab_b) ?  
    reg_b_to_bus : 32'bz;
```

...

```
endmodule
```

 

# Reference

---

1. 教師自製
2. Modeling, Synthesis, and Rapid Prototyping with the Verilog HDL, Michael D. Ciletti, ISBN: 0139773983, Prentice Hall, 1999.

