

硬體描述語言

Chapter 05



Synthesis of Sequential Logic and Language Construct

Ren-Der Chen (陳仁德)

Department of Computer Science and
Information Engineering

National Changhua University of Education

E-mail: rdchen@cc.ncue.edu.tw

Fall, 2024

Synthesis of Sequential Logic with Latches (1/2)

- Latches are synthesized
 - Intentionally
 - Accidentally
- Latch-free logic
 - A feedback-free netlist of combinational primitives will synthesize into latch-free combinational logic.
 - A set of feedback-free continuous assignments will synthesize into latch-free combinational logic.
 - A description of combinational logic must assign value to the outputs for *all* possible values of the inputs.

Synthesis of Sequential Logic with Latches (2/2)

■ Latch-inferred logic

- A **continuous assignment** using a conditional operator with feedback will synthesize into a latch.

Ex. **assign** data_out = (CS_b == 0) ?

(WE_b == 0) ? data_in : data_out : 1'bz;

- *Transparent mode* (CB_b == 0 and WE_b == 0): data_out follows data_in.
- *Latched mode* (CB_b == 0 and WE_b == 1): data_out = data_out.
- *Three-state, high-impedance* (CB_b == 1).

Synthesis of Latches (1/3)

- Latch is **level-sensitive**.
- The output is affected by the input only when a **control signal** is asserted.
- At other times, the input is ignored and the output retains its residual value.
- A **latch** is inferred by the synthesis tool when it detects a level-sensitive behavior in which a register variable is assigned value in some threads of activity, **but not others** (e.g., an incomplete **if** statement).

Synthesis of Latches (2/3)

- If the activity flow assigns value to a given register variable in all possible threads of the activity, a latch will be inferred if a path assigns a variable its own value, i.e., **self-feedback**.
- In synthesis, latches implement incompletely-specified assignments to register variables in **case** and **if** statements in a **level-sensitive** cyclic behavior.
- If a **case** statement has a default assignment with feedback (the variable is explicitly assigned to itself), the synthesis tool will choose a **mux** structure with feedback.

Synthesis of Latches (3/3)

- If the behavior is **edge-sensitive**, incomplete **case** and **if** statements synthesize register variable to **flip-flops**.
- If the statements are completed with feedback, the result is a register whose output is fed back through a **mux** at its data path.
- The functionality of a latch is also inferred when the conditional operator (**? ... :**) is implemented with feedback.

Synthesis of Latches - case (1/3)

```
module latch_case_assign (latch_in, enable, set, clear, latch_out);  
    input          latch_in, enable, set, clear;  
    output         latch_out;  
    reg            latch_out;  
    // Efficient in simulation, but does not synthesize with some tools  
    always @ (enable or set or clear)  
        case ({enable, set, clear})  
            3'b100: assign latch_out = latch_in;    // Transparent mode  
            3'b110: assign latch_out = 1'b1;        // Set  
            3'b010: assign latch_out = 1'b1;        // Set  
            3'b101: assign latch_out = 1'b0;        // Clear  
            3'b001: assign latch_out = 1'b0;        // Clear  
            default: deassign latch_out;            // Holds residual value  
        endcase  
endmodule
```

Synthesis of Latches - case (2/3)

```
module latch_case1 (latch_in, enable, set, clear, latch_out);
    input          latch_in, enable, set, clear;
    output         latch_out;
    reg            latch_out;
    // Less efficient in simulation, but can be synthesized by all tools
    always @ (latch_in or enable or set or clear)
        case ({enable, set, clear})
            3'b100: latch_out = latch_in;    // Transparent mode
            3'b110: latch_out = 1'b1;        // Set
            3'b010: latch_out = 1'b1;        // Set
            3'b101: latch_out = 1'b0;        // Clear
            3'b001: latch_out = 1'b0;        // Clear
            default: latch_out = latch_out;  // Holds residual value
        endcase // The case statement is completed with default feedback.
endmodule
```


Synthesis of Latches - case (3/3)

```
module latch_case2 (latch_in, enable, set, clear, latch_out);
```

```
    input          latch_in, enable, set, clear;
```

```
    output         latch_out;
```

```
    reg            latch_out;
```

**All the three designs exhibit
correct transparent behavior!**

```
    always @ (latch_in or enable or set or clear)
```

```
        case ({enable, set, clear})
```

```
            3'b100: latch_out = latch_in;    // Transparent mode
```

```
            3'b110: latch_out = 1'b1;        // Set
```

```
            3'b010: latch_out = 1'b1;        // Set
```

```
            3'b101: latch_out = 1'b0;        // Clear
```


```
            3'b001: latch_out = 1'b0;        // Clear
```

```
            // No default value
```


```
        endcase // Incompletely-specified case statement => latch
```

```
endmodule
```

Synthesis Results

 

latch_case1

 

latch_case2

Under some specific synthesis tool and technology

Synthesis of Latches - if (1/3)

```
module latch_if_assign (data_in, latch_enable, data_out);  
    input        [3:0]    data_in;  
    input                latch_enable;  
    output       [3:0]    data_out;  
    reg          [3:0]    data_out;  
  
    always @ (latch_enable)  
        if (latch_enable)  
            assign      data_out = data_in;  
        else  
            deassign    data_out;  
  
endmodule
```

Synthesis of Latches - if (2/3)

```
module latch_if1 (data_in, latch_enable, data_out);
```

```
    input      [3:0]    data_in;
```

```
    input                      latch_enable;
```

```
    output     [3:0]    data_out;
```

```
    reg        [3:0]    data_out;
```

```
    // Designed with feedback
```

```
    always @ (data_in or latch_enable)
```


```
        if (latch_enable)
```

```
            data_out = data_in;
```

```
        else
```

```
            data_out = data_out;
```

```
endmodule
```

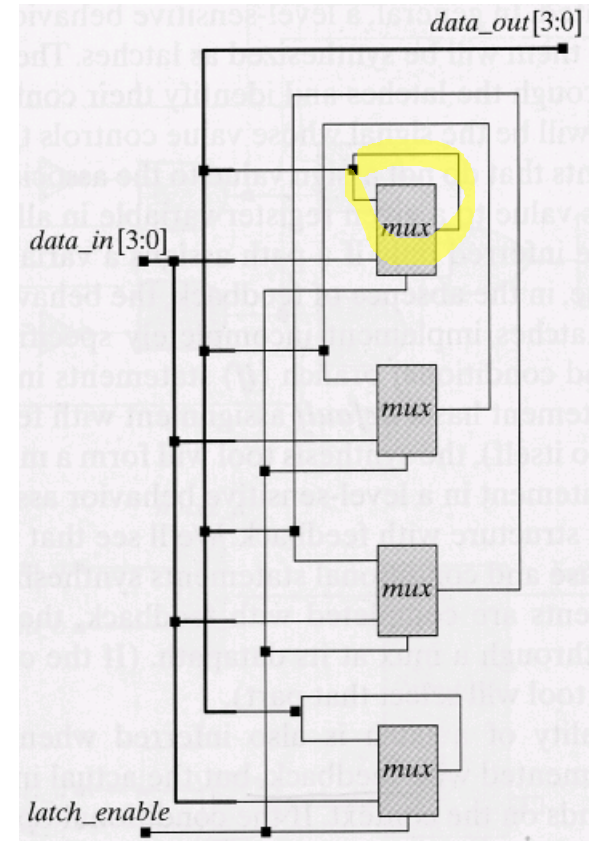

```
assign data_out[3:0] = latch_enable ? data_in[3:0] : data_out[3:0];
```

Synthesis of Latches - if (3/3)

```
module latch_if2 (data_in, latch_enable, data_out);
```

```
    input        [3:0]    data_in;
```

```
    input                latch_enable;
```

```
    output       [3:0]    data_out;
```

```
    reg          [3:0]    data_out;
```


```
    // Incompletely specified
```

```
    always @ (data_in or latch_enable)
```

```
        if (latch_enable)
```

```
            data_out = data_in;
```

```
endmodule
```

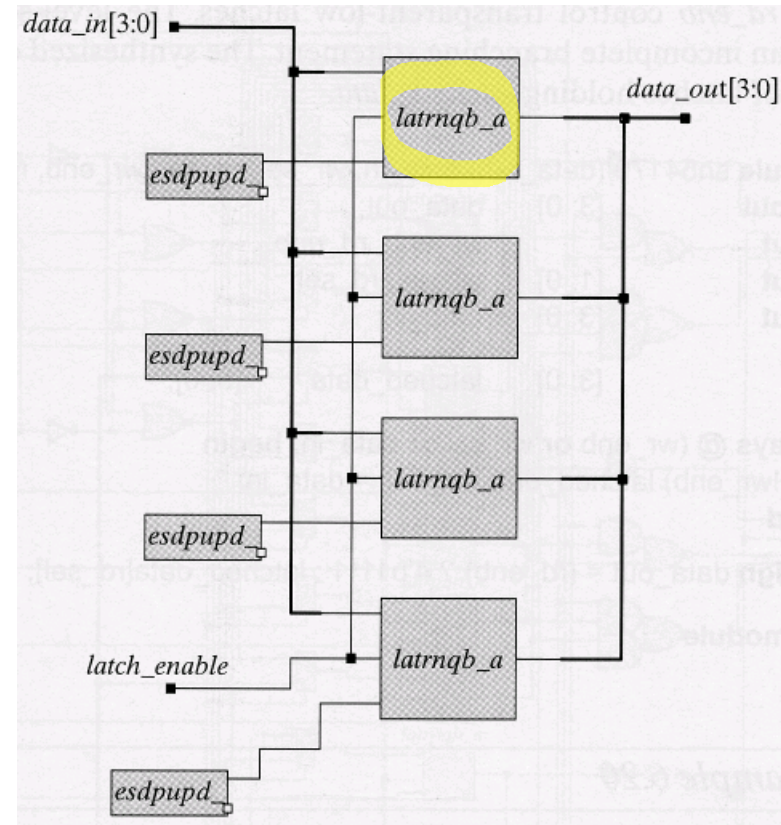

Latch_if1 and latch_if2 are equivalent in simulation, but the physical circuit will have different area/speed trade-offs.

A Four-Bit OR Gate without Latch

```
module or4_behav (x_in, y);
    parameter    word_length = 4;
    input        [word_length-1:0] x_in;
    output       y;
    reg          y;
    integer      k;

    always @ (x_in) begin: check_for_1
        y = 0;
        for (k = 0; k <= word_length - 1; k = k+1)
            if (x_in[k] == 1) begin
                y = 1;
                disable check_for_1;
            end
        end
    end
endmodule
```

A Four-Bit OR Gate with Latched Output



```
module or4_behav_latch (x_in, y);  
    parameter    word_length = 4;  
    input        [word_length-1:0] x_in;  
    output       y;  
    reg          y;  
    integer      k;
```



Accidental synthesis of latches !!

```
    always @ (x_in [3:1]) begin: check_for_1  
        y = 0;  
        for (k = 0; k <= word_length - 1; k = k+1)  
            if (x_in[k] == 1) begin  
                y = 1;  
                disable check_for_1;  
            end  
        end  
    end  
endmodule
```

Synthesis and Simulation Results

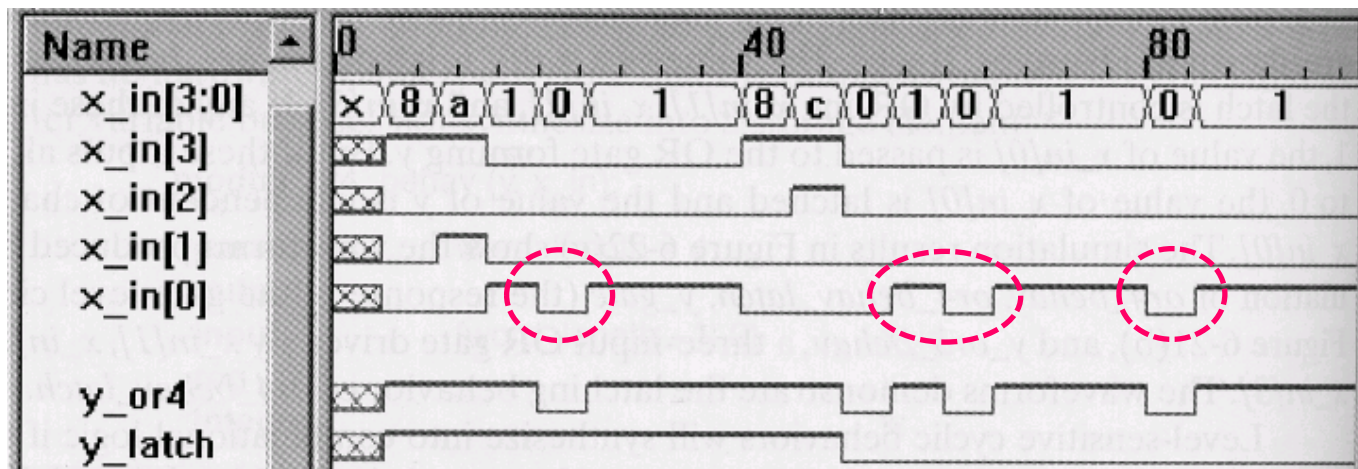 

Two Flip-Flops for Swapping Values

```
module swap_synch (clk, set1, set2, data_a, data_b);
```

```
  input          clk, set1, set2;
```

```
  output         data_a, data_b;
```

```
  reg            data_a, data_b;
```

```
  always @ (posedge clk) begin
```

```
    if (set1) begin
```

```
      data_a <= 0; data_b <= 1;
```

```
    end
```

```
    else if (set2) begin
```

```
      data_a <= 1; data_b <= 0;
```

```
    end
```


```
    else begin
```

```
      data_b <= data_a; data_a <= data_b;
```

```
    end
```

```
  end
```

```
endmodule
```

 

- A register variable will be synthesized as the output of a flip-flop when its value is assigned synchronously with *the edge of a signal*. (edge-triggered)

Four-Bit Register (1/2)

```
module D_reg4_a (Data_in, clock, reset, Data_out);
```

```
    input          [3:0]    Data_in;
```

```
    input          clock, reset;
```

```
    output         [3:0]    Data_out;
```

```
    reg            [3:0]    Data_out;
```

```
    always @ (posedge clock or posedge reset)
```


```
    if (reset == 1'b1)
```

```
        Data_out <= 4'b0;
```

```
    else
```

```
        Data_out <= Data_in;
```

```
endmodule
```

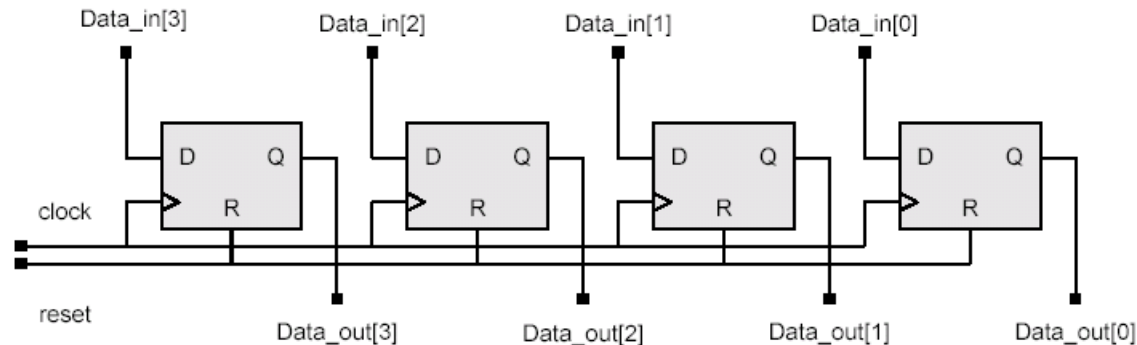


Four-Bit Register (2/2)

```
module D_reg4_b (Data_in, clock, reset, Data_out);  
    input        [3:0]    Data_in;  
    input                    clock, reset;  
    output       [3:0]    Data_out;  
    reg          [3:0]    Data_out;  
  
    always @ (posedge clock)  
        Data_out <= Data_in;  
    always @ (reset)  
        if (reset)  
            assign Data_out = 4'b0;  
        else  
            deassign Data_out;  
endmodule
```

**Maybe an unsupported
description !!**


JK Flip-Flops (1/2)

```
module jk_flop_1 (j, k, clock, rst, q, qb);  
    input          j, k, clock, rst;  
    output         q, qb;  
    reg            q;  
    assign         qb = ~q;  
  
    always @ (posedge clock or posedge rst) begin  
        if (rst == 1'b1) q = 1'b0;  
        else if (j == 1'b0 && k == 1'b0) q = q;  
        else if (j == 1'b0 && k == 1'b1) q = 1'b0;  
        else if (j == 1'b1 && k == 1'b0) q = 1'b1;  
        else if (j == 1'b1 && k == 1'b1) q = ~q;  
    end  
endmodule
```

 

JK Flip-Flops (2/2)


```
module jk_flop_2 (j, k, clock, rst, q, qb);  
  input          j, k, clock, rst;  
  output         q, qb;  
  reg            q;  
  assign         qb = ~q;  
  always @ (posedge clock or posedge rst) begin  
    if (rst == 1'b1)  
      q = 1'b0;  
    else  
      case ({j, k})  
        2'b00: q = q;  
        2'b01: q = 1'b0;  
        2'b10: q = 1'b1;  
        2'b11: q = ~q;  
      endcase  
    end  
endmodule
```

 

Synthesis Result

case ({j, k})

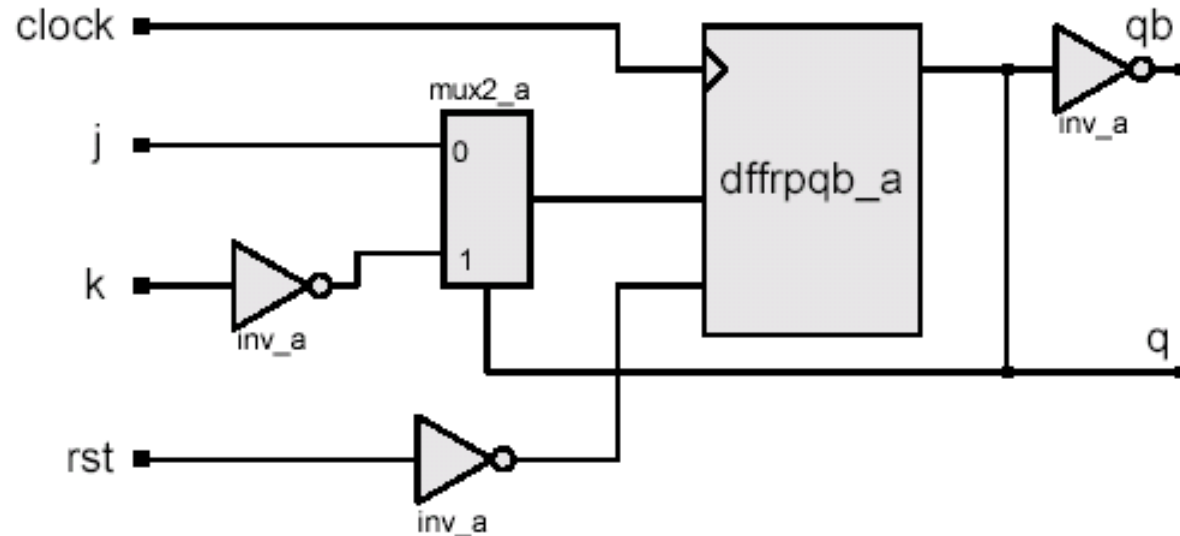2'b00: q = q;
2'b01: q = 1'b0;
2'b10: q = 1'b1;
2'b11: q = ~q;



The synthesis tool uses a D-type flip-flop with input logic to decode JK inputs.

Registered AND Gate

```
module reg_and (a, b, c, clk, y);
```

```
  input      a, b, c, clk;
```


```
  output     y;
```

```
  reg        y;
```

```
  always @ (posedge clk)
```

```
    y <= a & b & c;
```

```
endmodule
```

 

Registered Multiplexer

```
module mux_reg (a, b, c, d, select, clock, y);
```

```
  input          [7:0]    a, b, c, d;
```

```
  input          [1:0]    select;
```

```
  input          clock;
```

```
  output         [7:0]    y;
```

```
  reg            [7:0]    y;
```

```
  always @(posedge clock)
```

```
    case (select)
```

```
      0:    y <= a;
```

```
      1:    y <= b;
```


```
      2:    y <= c;
```

```
      3:    y <= d;
```

```
      default: y <= 8'bx;
```

```
    endcase
```

```
endmodule
```

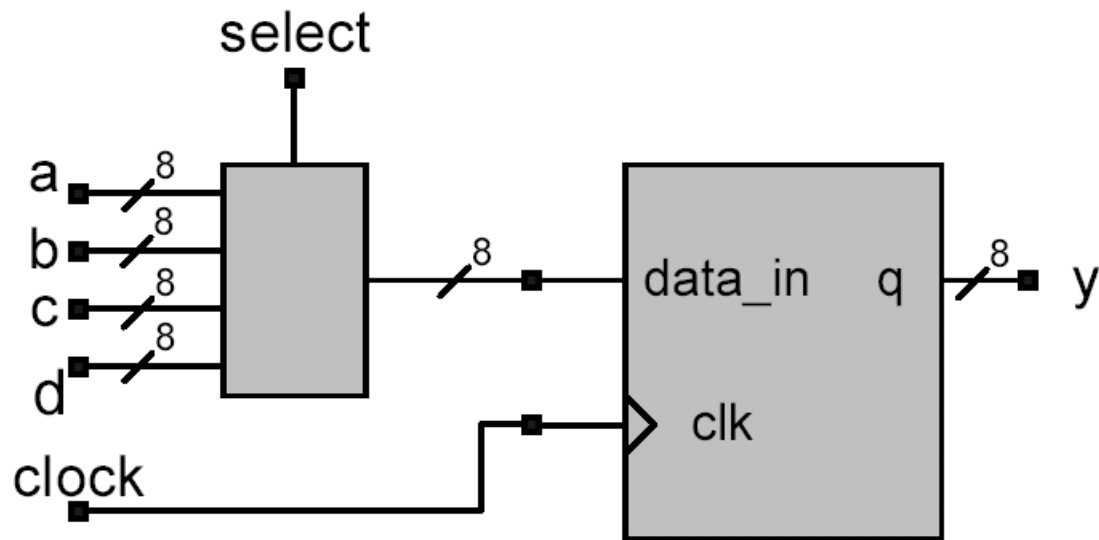

Physical Size from Synthesis

- The physical size of an ASIC synthesized from Verilog is not necessarily proportional to the size of the source code.

```
always @ (posedge clock) begin
```


```
    data_register <= data_bus;
```

```
end
```

- `data_register` could be a single bit or a 32-bit register.
- The physical part selected in the technology mapping depends on the robustness of the target library.

Shift Register 1
 
```
module Shift_reg4_1_1 (Data_in, clock, reset, Data_out);  
  input      Data_in, clock, reset;  
  output     Data_out;  
  reg        [3:0] Data_reg;  
  
  assign     Data_out = Data_reg[0];  
  
  always @ (posedge clock or negedge reset)  
    if (reset == 1'b0) Data_reg <= 4'b0;  
    else Data_reg <= {Data_in, Data_reg[3:1]};  
  
endmodule
```




Shift Register 2

```
module Shift_reg4_1_2 (Data_in, clock, reset, Data_out);
```

```
  input      Data_in, clock, reset;
```

```
  output     Data_out;
```

```
  reg       [3:0] Data_reg;
```

 

```
  assign     Data_out = Data_reg[0];
```

```
  always @ (posedge clock or negedge reset)
```

```
    if (reset == 1'b0) Data_reg <= 4'b0;
```

```
    else begin // in the order of row by row
```

```
      Data_reg[3] <= Data_in;    Data_reg[2] <= Data_reg[3];
```

```
      Data_reg[1] <= Data_reg[2]; Data_reg[0] <= Data_reg[1];
```

```
    end
```

```
endmodule
```

Shift Register 3

```
module Shift_reg4_2_2 (Data_in, clock, reset, Data_out);
```

```
    input          Data_in, clock, reset;
```

```
    output         Data_out;
```

```
    reg    [3:0] Data_reg;
```

```
    assign      Data_out = Data_reg[0];
```

```
    always @ (posedge clock or negedge reset)
```

```
        if (reset == 1'b0) Data_reg = 4'b0;
```


```
        else begin // in the order of row by row
```

```
            Data_reg[3] = Data_in;      Data_reg[2] = Data_reg[3];
```

```
            Data_reg[1] = Data_reg[2];  Data_reg[0] = Data_reg[1];
```

```
        end
```

```
    endmodule
```

 

Only one register is synthesized!

Parallel Load Register (1/2)

```
module Par_load_reg4_1_1 (Data_in, load, clock, reset, Data_out);  
  input          [3:0]    Data_in;  
  input          load, clock, reset;  
  output         [3:0]    Data_out;  
  reg            [3:0]    Data_out;
```

```
  always @ (posedge clock or posedge reset)  
    if (reset == 1'b1)  
      Data_out <= 4'b0;  
    else if (load == 1'b1)  
      Data_out <= Data_in;  
endmodule
```

```
always @ (posedge clock or posedge reset)  
  if (reset == 1'b1)  
    Data_out = 4'b0;  
  else if (load == 1'b1)  
    Data_out = Data_in;
```

Parallel Load Register (2/2)

```
always @ (posedge clock or posedge reset)
```

```
  if (reset == 1'b1)
```

```
    Data_out <= 4'b0;
```

```
  else if (load == 1'b1) begin
```

```
    Data_out[3] <= Data_in[3];
```

```
    Data_out[2] <= Data_in[2];
```

```
    Data_out[1] <= Data_in[1];
```

```
    Data_out[0] <= Data_in[0];
```

```
  end
```

```
always @ (posedge clock or posedge reset)
```

```
  if (reset == 1'b1)
```

```
    Data_out = 4'b0;
```

```
  else if (load == 1'b1) begin // in the order of row by row
```

```
    Data_out[3] = Data_in[3];
```


```
    Data_out[2] = Data_in[2];
```

```
    Data_out[1] = Data_in[1];
```

```
    Data_out[0] = Data_in[0];
```

```
  end
```

Synthesis Result

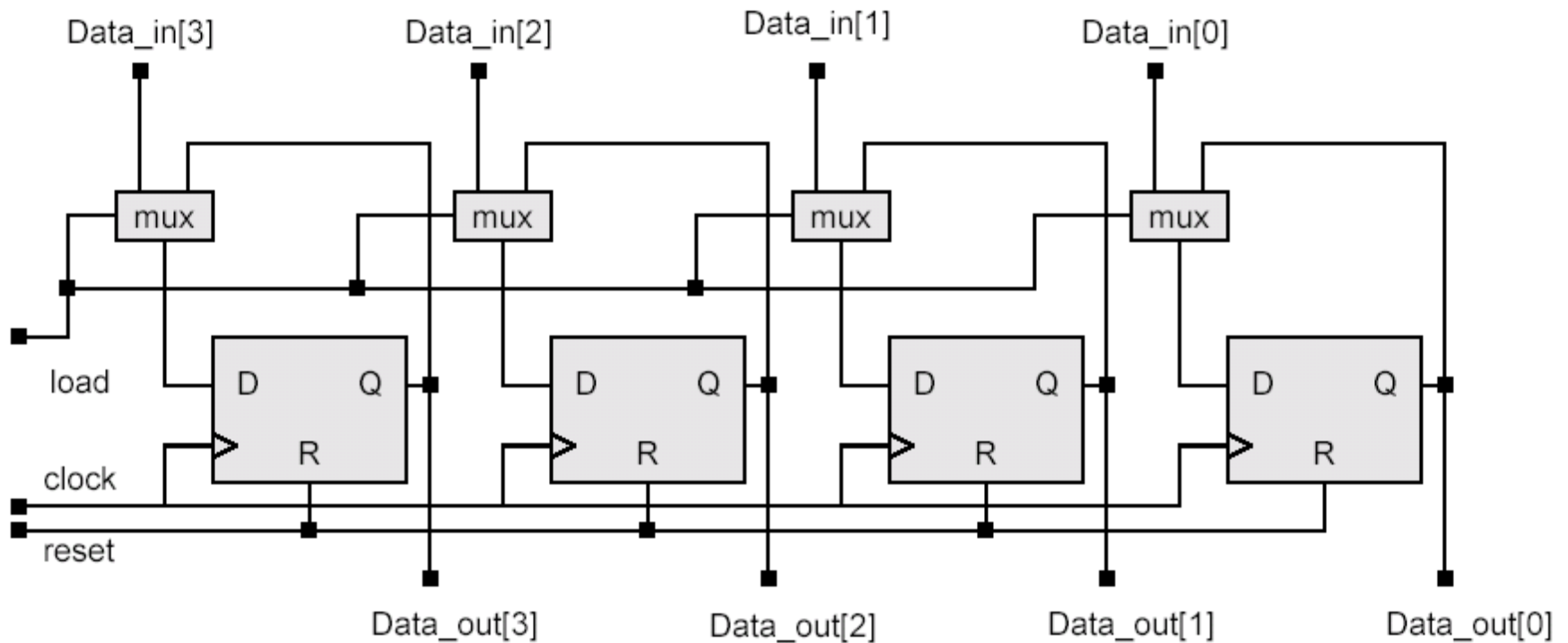

Barrel Shifter

```
module barrel_shifter (Data_in, load, clock, reset, Data_out);
```

```
  input          [7:0]    Data_in;
```

```
  input          load, clock, reset;
```

```
  output         [7:0]    Data_out;
```

```
  reg           [7:0]    Data_out;
```

```
  always @ (posedge clock or posedge reset)
```

```
    if (reset == 1'b1)
```

```
      Data_out <= 8'b0;
```


```
    else if (load == 1'b1)
```

```
      Data_out <= Data_in;
```


```
    else
```

```
      Data_out <= {Data_out[6:0], Data_out[7]};
```

```
endmodule
```

 

Synthesis Result

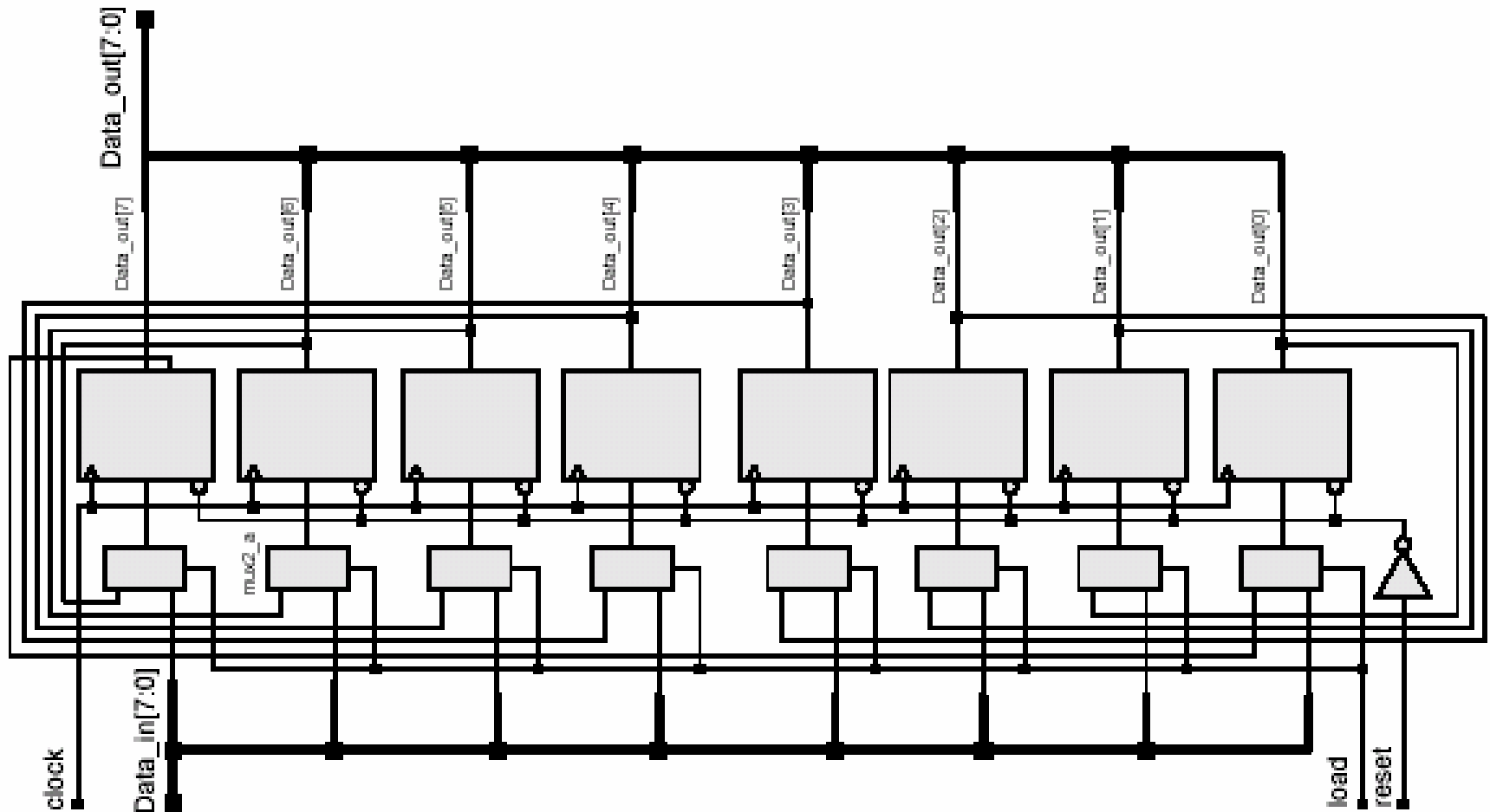

Under some specific synthesis tool and technology

Ripple Counter (1/2)

```
module ripple_counter (toggle, clock, reset, count);
    input                toggle, clock, reset;
    output [3:0]         count;
    reg [3:0]            count;
    wire                c0, c1, c2;

    assign c0 = count[0], c1 = count[1], c2 = count[2];

    always @ (posedge clock or posedge reset)
        if (reset == 1'b1) count[0] <= 1'b0;
        else if (toggle == 1'b1) count[0] <= ~count[0];
```

0000
0001
0010
0011
0100
0101
0110
0111
1000
1001
1010
1011
1100
1101
1110
1111
0000
...

Ripple Counter (2/2)

```
always @ (negedge c0 or posedge reset)
    if (reset == 1'b1)        count[1] <= 1'b0;
    else if (toggle == 1'b1) count[1] <= ~count[1];


always @ (negedge c1 or posedge reset)
    if (reset == 1'b1)        count[2] <= 1'b0;
    else if (toggle == 1'b1) count[2] <= ~count[2];

always @ (negedge c2 or posedge reset)
    if (reset == 1'b1)        count[3] <= 1'b0;
    else if (toggle == 1'b1) count[3] <= ~count[3];

endmodule
```

0000
0001
0010
0011
0100
0101
0110
0111
1000
1001
1010
1011
1100
1101
1110
1111
0000
...

Synthesis Result

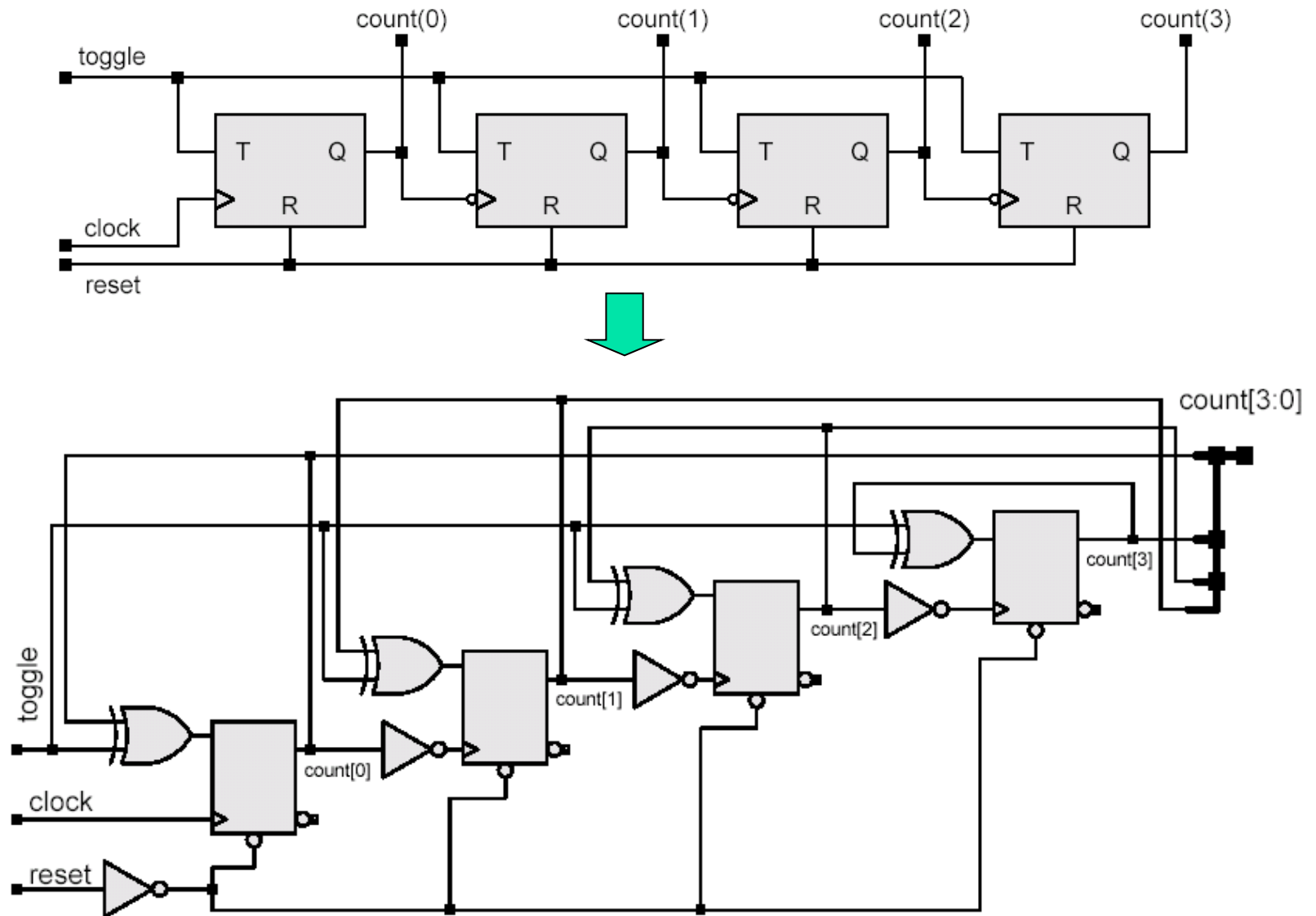

Ring Counter

```
module ring_counter (enable, clock, reset, count);
```

```
    input                enable, clock, reset;
```

```
    output      [7:0]    count;
```

```
    reg         [7:0]    count;
```

```
    always @ (posedge clock or  
              posedge reset)
```


```
        if (reset == 1'b1)
```

```
            count <= 8'b0000_0001;
```

```
        else if (enable == 1'b1)
```


```
            count <= {count[6:0], count[7]};
```

```
endmodule
```

 


Up-Down Counter

```
module up_down_counter (load, count_up, counter_on, clk, reset, Data_in, Count);  
  input                                load, count_up, counter_on, clk, reset;  
  input      [2:0]      Data_in;  
  output      [2:0]      Count;  
  reg         [2:0]      Count;  
  
  always @ (posedge clk or posedge reset)  
    if (reset == 1'b1)      Count = 3'b0;  
    else if (load == 1'b1)  Count = Data_in;  
    else if (counter_on == 1'b1) begin  
      if (count_up == 1'b1)  
        Count = Count + 1;  
      else  
        Count = Count - 1;  
    end  
endmodule
```

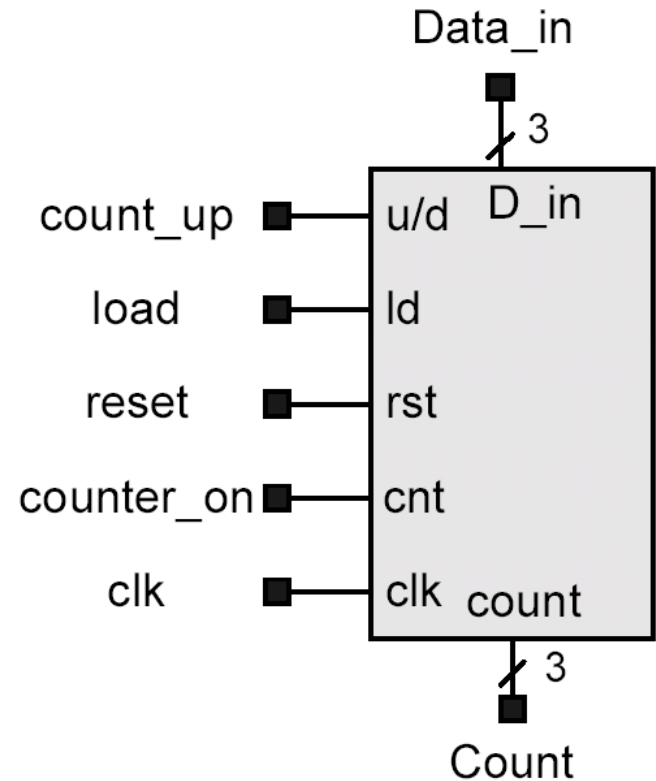

Synthesis Result

 


Under some specific synthesis tool and technology

Shift Register

```
always @ (posedge clock)  
  if (reset == 1'b1) begin  
    reg_a <= 1'b0;  
    reg_b <= 1'b0;  
    reg_c <= 1'b0;  
    reg_d <= 1'b0;  
  end  
end
```

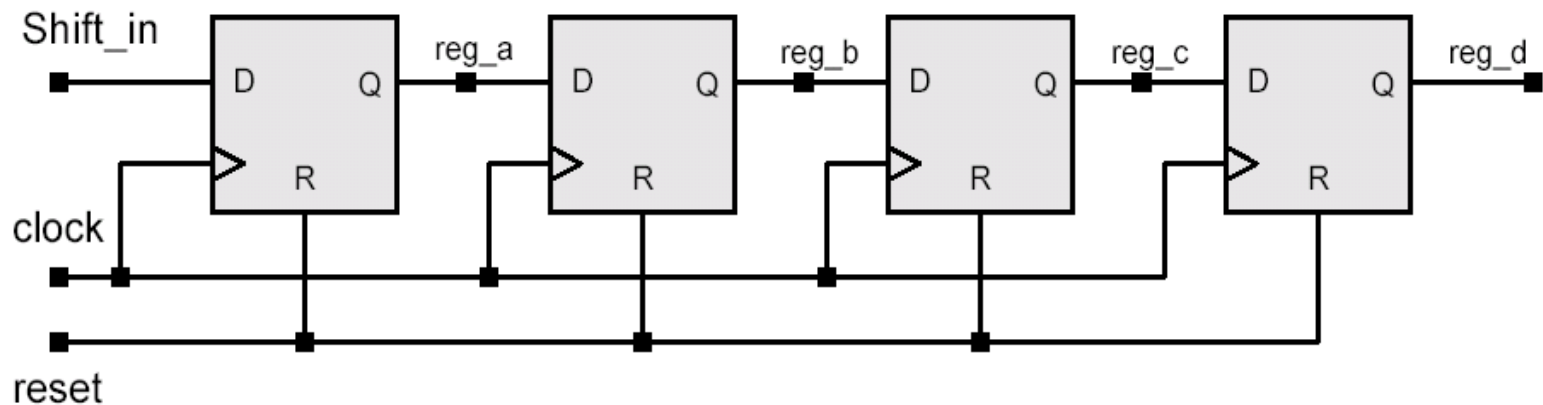
```
else begin  
  reg_a <= Shift_in;  
  reg_b <= reg_a;  
  reg_c <= reg_b;  
  reg_d <= reg_c;  
end
```



Shift Register with Registered Combinational Logic (1/4)

```
module shifter_1 (Data_in, clock, reset, sig_d, new_signal);  
  input          Data_in, clock, reset;  
  output         sig_d, new_signal;  
  reg           sig_a, sig_b, sig_c, sig_d, new_signal;  
  
  always @ (posedge clock or posedge reset) begin  
  
    if (reset == 1'b1) begin  
      sig_a <= 0;  
      sig_b <= 0;  
      sig_c <= 0;  
      sig_d <= 0;  
      new_signal <= 0;  
    end  
  
    else begin  
      sig_a <= Data_in;  
      sig_b <= sig_a;  
      sig_c <= sig_b;  
      sig_d <= sig_c;  
      new_signal <= (~ sig_a) & sig_b;  
    end  
  end  
endmodule
```

 Shift Register with Registered Combinational Logic (2/4)




An output that is assigned new value within a synchronized behavior will be synthesized as the output of a **flip-flop**.

Shift Register with Registered Combinational Logic (3/4)

```
module shifter_1 (Data_in, clock, reset, sig_d, new_signal);  
  input          Data_in, clock, reset;  
  output         sig_d, new_signal;  
  reg            sig_a, sig_b, sig_c, sig_d; wire new_signal;  
  
  always @ (posedge clock or posedge reset) begin  
  
    if (reset == 1'b1) begin  
      sig_a <= 0;  
      sig_b <= 0;  
      sig_c <= 0;  
      sig_d <= 0;  
      new_signal <= 0;  
    end  
  
    else begin  
      sig_a <= Data_in;  
      sig_b <= sig_a;  
      sig_c <= sig_b;  
      sig_d <= sig_c;  
    end  
  
    end  
  
    assign new_signal <= (~ sig_a) & sig_b;  
endmodule
```

 Shift Register with Registered Combinational Logic (4/4)




Signals that are assigned new values outside a behavior or in a behavior that does not include a synchronizing signal in its event control expression will be synthesized as **combinational logic**.

Data Shifter (1/2)


```
module data_shift ( data_out, data_in, clk, data_load, SL, SR);  
  input    [3:0] data_in;  
  input      clk, data_load, SL, SR;  
  output  [3:0] data_out;  
  
  reg      [3:0] data_out;  
  
  always @ (posedge clk)  
    if (data_load) data_out = data_in;  
    else if (SL) data_out = data_out << 1;  
    else if (SR) data_out = data_out >> 1;  
endmodule
```

Data Shifter (2/2)

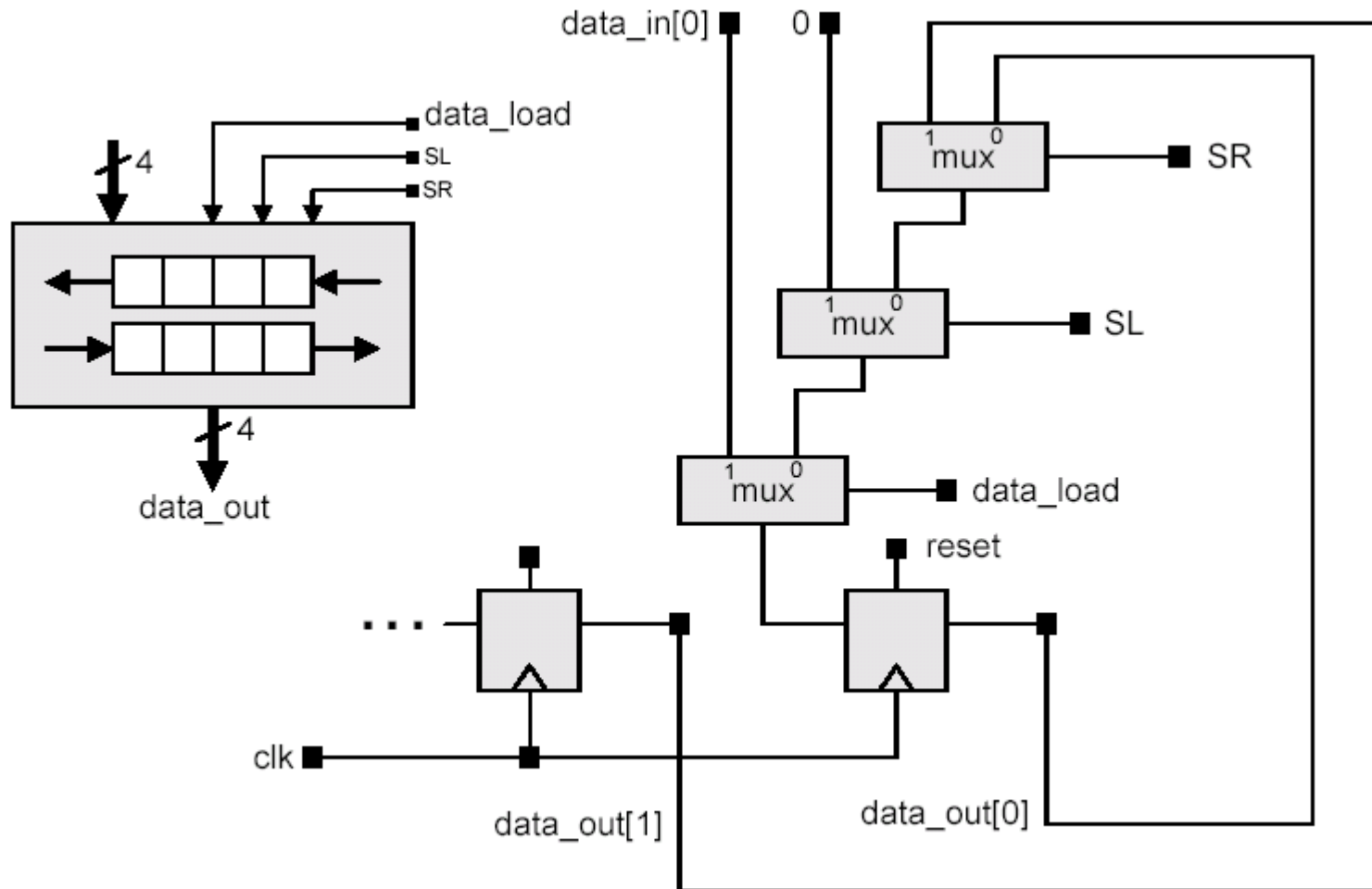

Data path for LSB

Synthesis Result

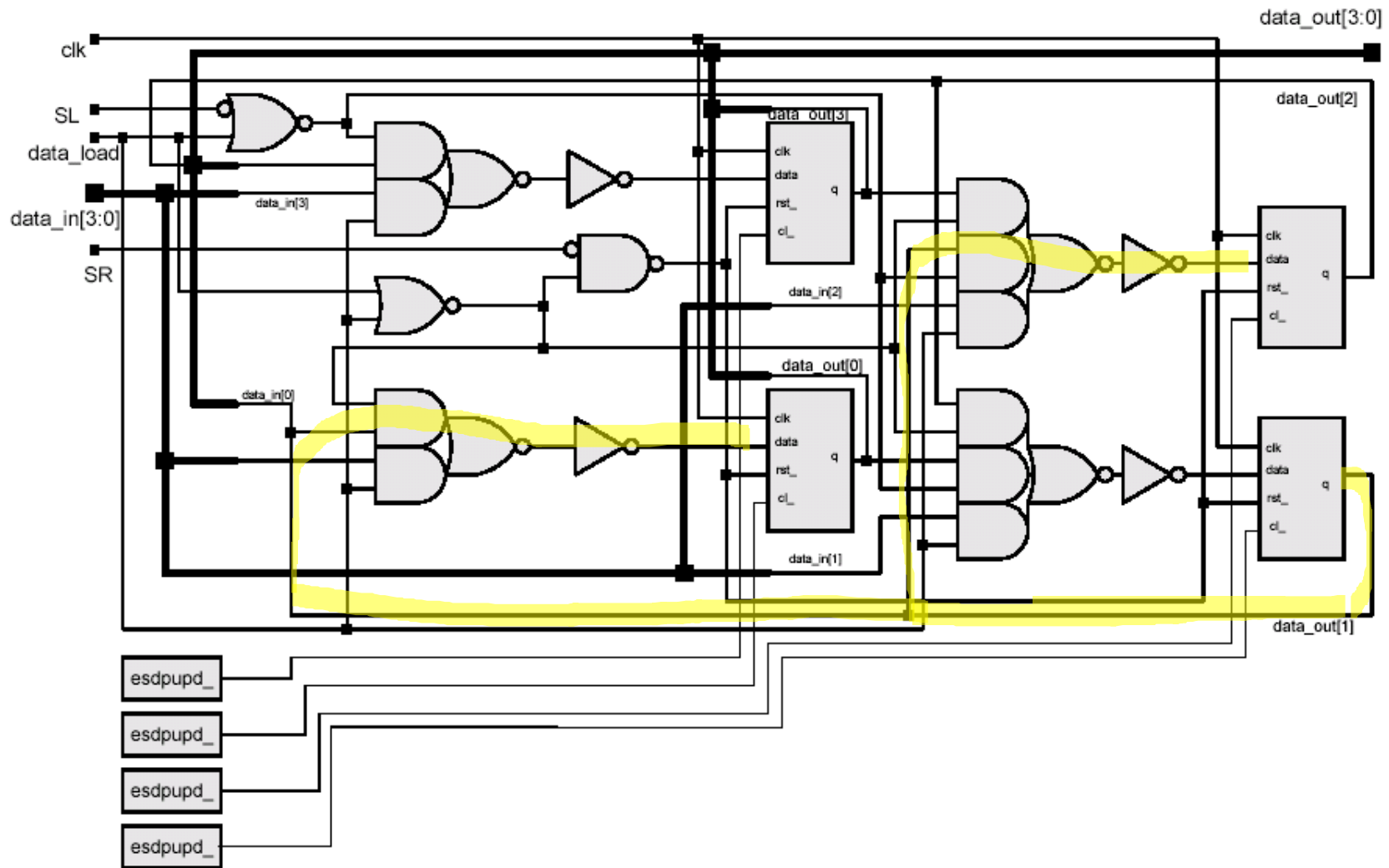

Accumulator 1

```
module Add_Accum_1 (data, enable, clk, reset_b, overflow, accum);  
    input          [3:0]    data;  
    input          enable, clk, reset_b;  
    output         overflow;  
    output        [3:0]    accum;  
    reg           overflow;  
    reg          [3:0]    accum;  
  
    always @ (posedge clk or negedge reset_b)  
        if (reset_b == 0) begin overflow <= 0; accum <= 0; end  
        else if (enable) {overflow, accum} <= accum + data;  
endmodule
```

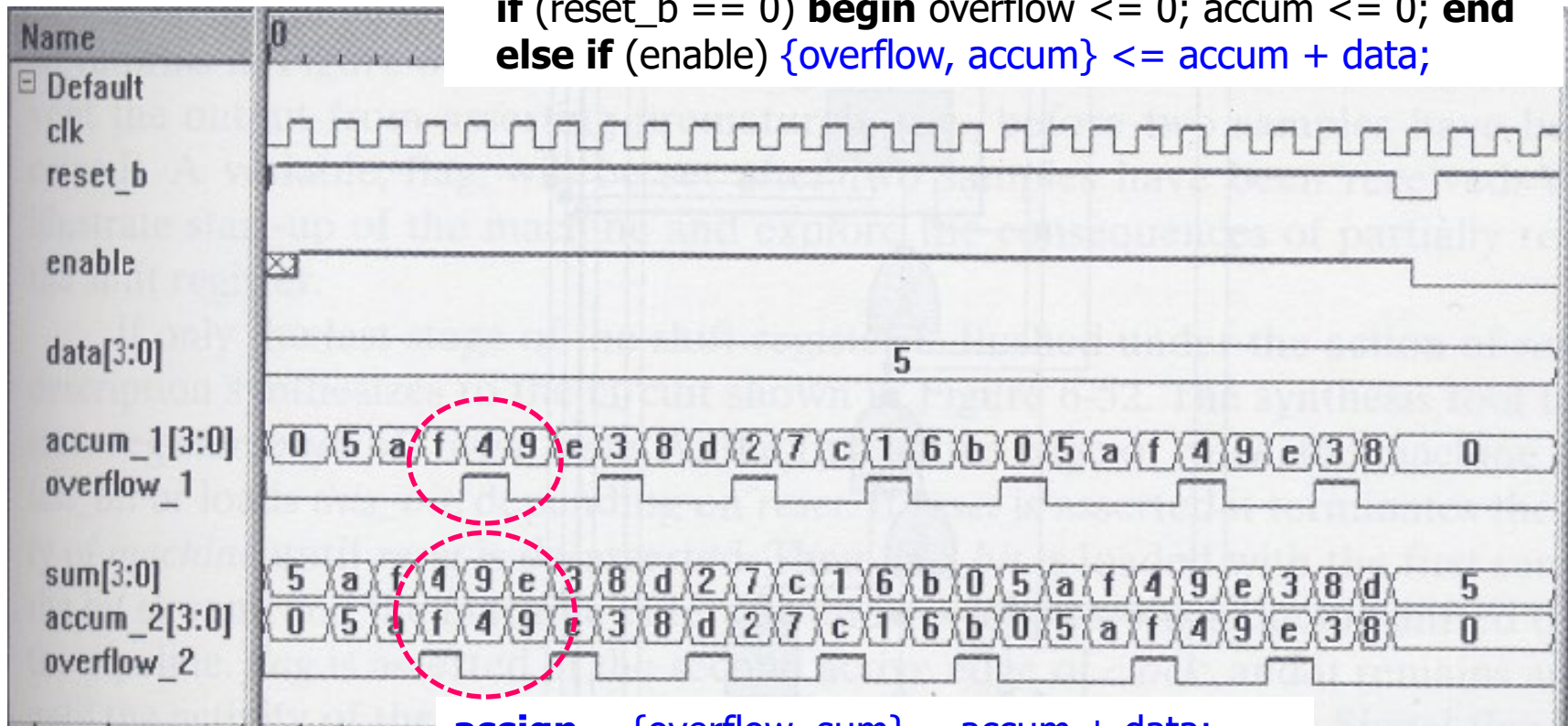

Accumulator 2

```
module Add_Accum_2 (data, enable, clk, reset_b, overflow, accum);  
    input          [3:0]    data;  
    input          enable, clk, reset_b;  
    output         overflow;  
    output [3:0]    accum;  
    reg           [3:0]    accum;  
    wire          overflow;  
    wire [3:0]    sum;  
    assign        {overflow, sum} = accum + data;  
    always @ (posedge clk or negedge reset_b)  
        if (reset_b == 0) begin accum <= 0; end  
        else if (enable) accum <= sum;  
endmodule
```

Simulation Result

```

always @ (posedge clk or negedge reset_b)
  if (reset_b == 0) begin overflow <= 0; accum <= 0; end
  else if (enable) {overflow, accum} <= accum + data;
  
```



```

assign {overflow, sum} = accum + data;
always @ (posedge clk or negedge reset_b)
  if (reset_b == 0) begin accum <= 0; end
  else if (enable) accum <= sum;
  
```

Expression Substitution 1

```
module multiple_reg_assign
  (data_out1, data_out2, data_a, data_b, data_c, data_d, sel, clk);

  output [4:0] data_out1, data_out2;
  input  [3:0] data_a, data_b, data_c, data_d;
  input          clk;

  reg [4:0] data_out1, data_out2;

  always @ (posedge clk)
  begin
    data_out1 = data_a + data_b ;
    data_out2 = data_out1 + data_c;
    if (sel == 1'b0)
      data_out1 = data_out2 + data_d;
  end
endmodule
```

Expression Substitution 2

```
module expression_sub
  (data_out1, data_out2, data_a, data_b, data_c, data_d, sel, clk);


  output      [4:0] data_out1, data_out2;
  input       [3:0] data_a, data_b, data_c, data_d;
  input       clk, sel;
  reg         [4:0] data_out1, data_out2;

  always @ (posedge clk)
  begin
    data_out2 = data_a + data_b + data_c;
    if (sel == 1'b0)
      data_out1 = data_a + data_b + data_c + data_d;
    else
      data_out1 = data_a + data_b;
    end
  end
endmodule
```

```
data_out1 = data_a + data_b ;
data_out2 = data_out1 + data_c;
if (sel == 1'b0)
  data_out1 = data_out2 + data_d;
```


```
data_out2 = data_a + data_b + data_c;
if (sel == 1'b0)
  data_out1 = data_a + data_b + data_c + data_d;
else
  data_out1 = data_a + data_b;
```

Data Flow Graph

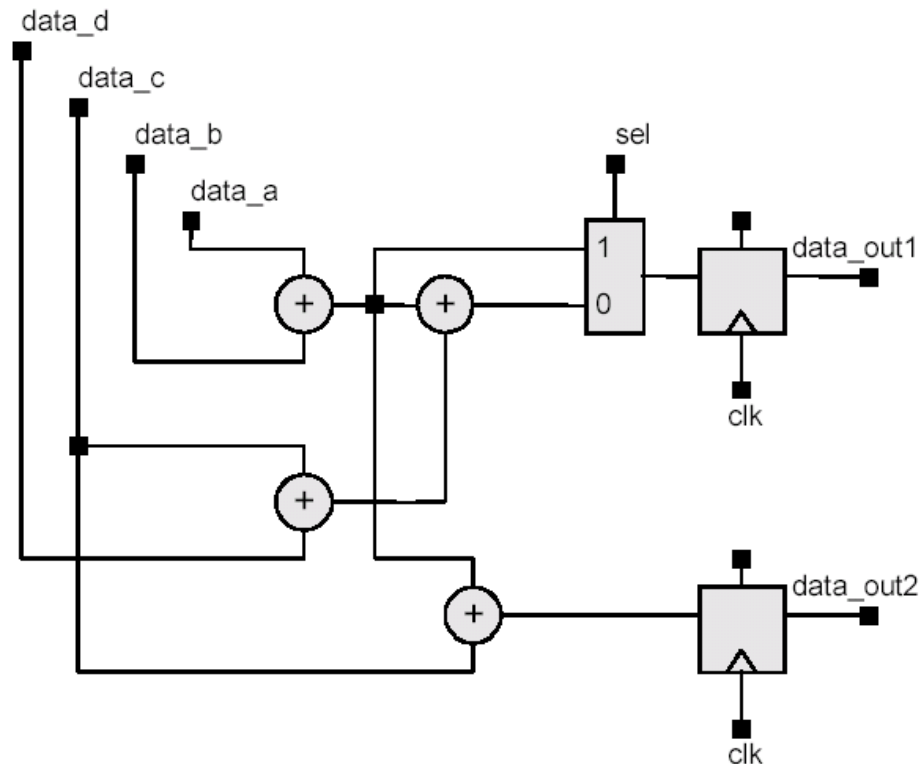

```
data_out2 = data_a + data_b + data_c;  
if (sel == 1'b0)  
    data_out1 = data_a + data_b + data_c + data_d;  
else  
    data_out1 = data_a + data_b;
```

Synthesis Result

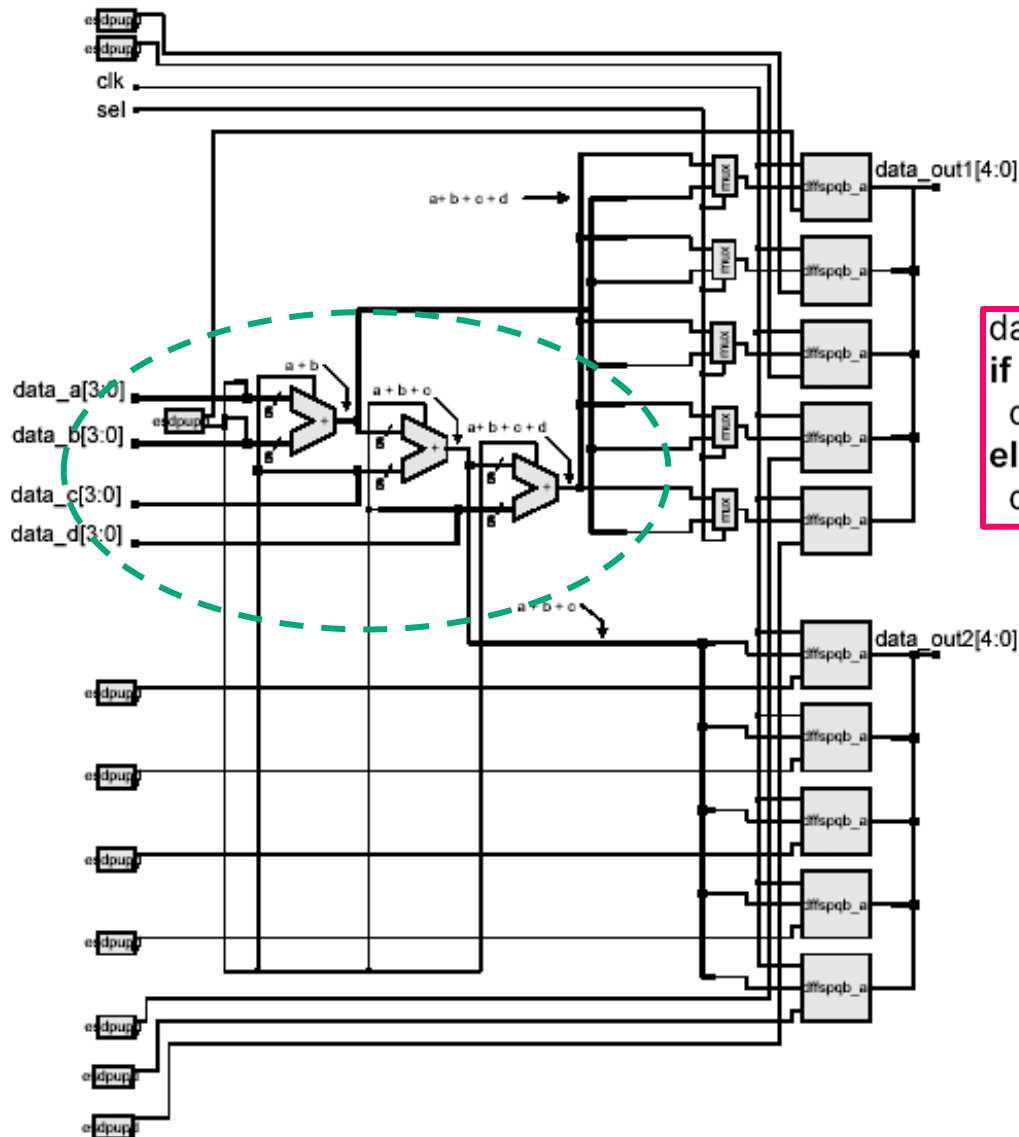

```
data_out2 = data_a + data_b + data_c;
if (sel == 1'b0)
    data_out1 = data_a + data_b + data_c + data_d;
else
    data_out1 = data_a + data_b;
```

Note: The adder units will be optimized, depending on the performance constraints and the available resources (e.g. carry look-ahead vs ripple-carry).


Synthesis of Non-Blocking Assignments

```
module pipe1 (data, rega, regb, regc, clk, reset);
  input      [1:0] data;
  input      clk, reset;
  output     [1:0] rega, regb, regc;
  reg       [1:0] rega, regb, regc;


  always @ (posedge clk or posedge reset)
    if (reset)
      begin
        rega = 2'b0;
        regb <= 2'b0;
        regc <= 2'b0;
      end
    else
      begin
        rega = data;
        regb <= rega + 1;
        regc <= regb + 1;
      end
    end
endmodule
```

Data Flow Graph and Synthesis Result

 Note: The data with non-blocking assignments implies a pipeline structure, and regc gets the value of regb from the previous cycle.


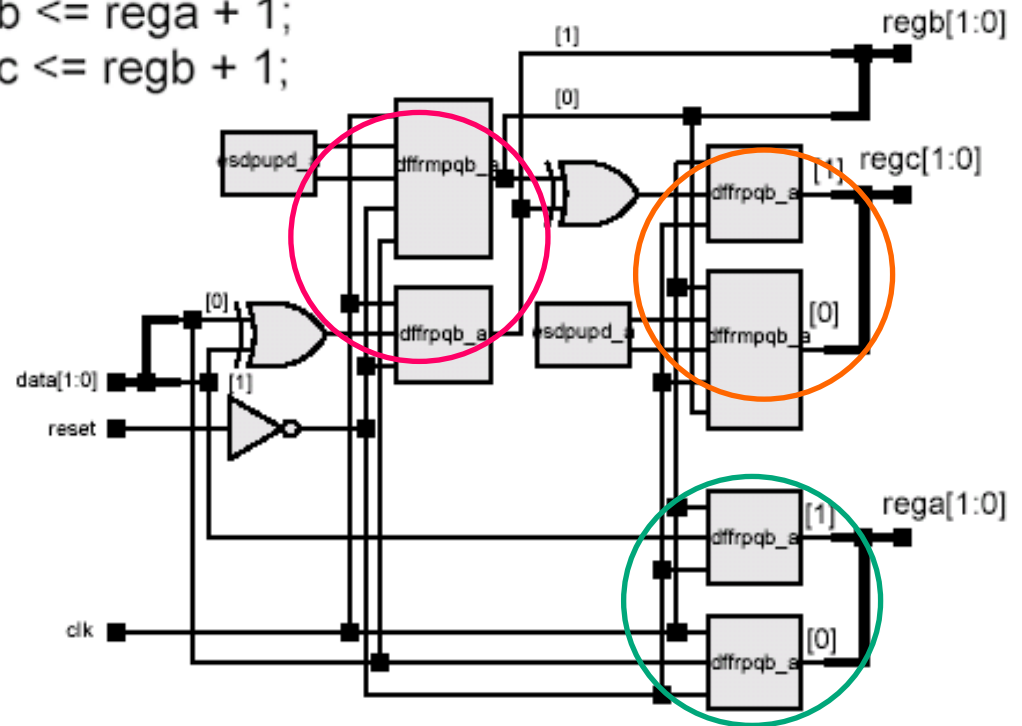
```
rega = data;  
regb <= rega + 1;  
regc <= regb + 1;
```




The activity associated with procedural assignments is processed before the activity associated with non-blocking assignments.

Synthesis of Non-Blocking Assignments

```
module pipe1_alt (data, rega, regb, regc, clk, reset);  
    input      [1:0] data;  
    input      clk, reset;  
    output     [1:0] rega, regb, regc;  
    reg        [1:0] rega, regb, regc;  
  
    always @ (posedge clk or posedge reset)  
        if (reset) rega = 2'b0; else rega = data;  
  
    always @ (posedge clk or posedge  
reset)  
        if (reset)  
            begin  
                regb <= 2'b0;  
                regc <= 2'b0;  
            end  
        else  
            begin  
                regb <= rega + 1;  
                regc <= regb + 1;  
            end  
        endmodule
```

Synthesis Result

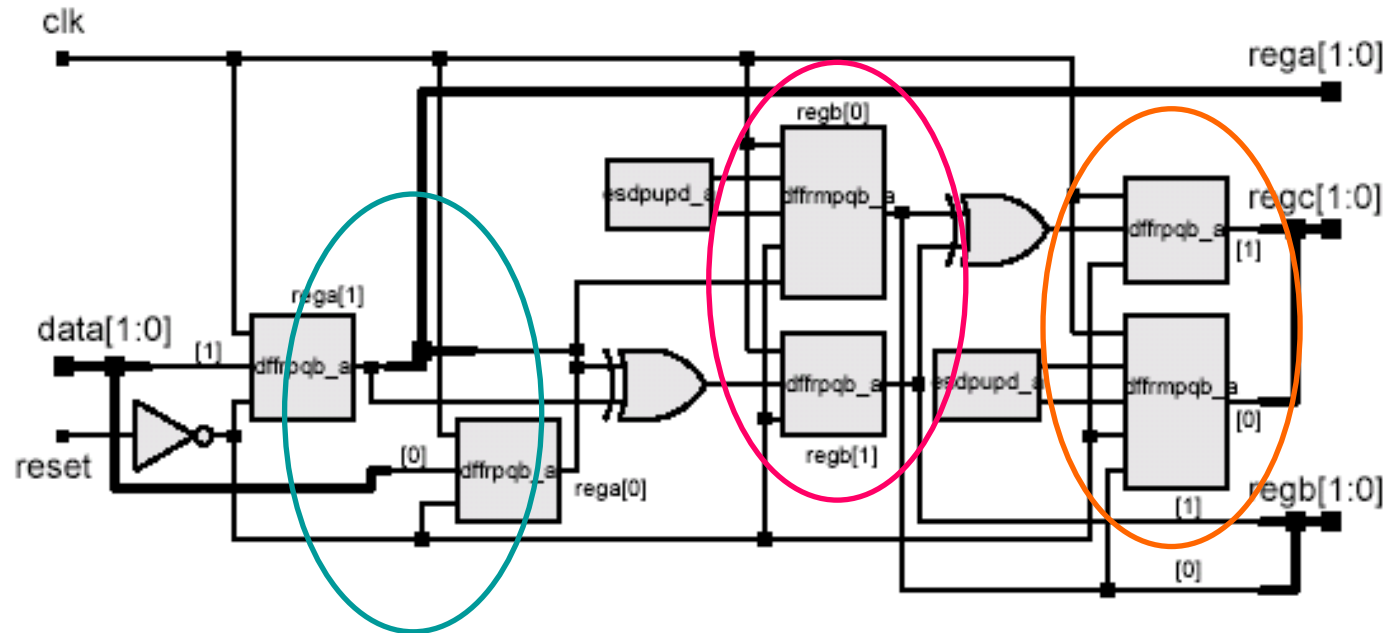

```
always @ (posedge clk or posedge reset)
  if (reset) rega = 2'b0; else rega = data;
```


```
regb <= rega + 1;
regc <= regb + 1;
```

Synthesis of Blocking Assignments


```
module pipe2 (data, rega, regb, regc, clk, reset);
  input      [3:0] data;
  input      clk, reset;
  output [3:0] rega, regb, regc;
  reg       [3:0] rega, regb, regc;

  always @ (posedge clk or posedge reset)
    if (reset)
      begin
        rega = 4'b0;
        regb = 4'b0;
        regc = 4'b0;
      end
    else
      begin
        rega = data;           // = data;
        regb = rega + 1;       // = data + 1;
        regc = regb + 1;       // = data + 1 + 1;
      end
    end
endmodule
```

Data Flow Graph and Synthesis Result

 


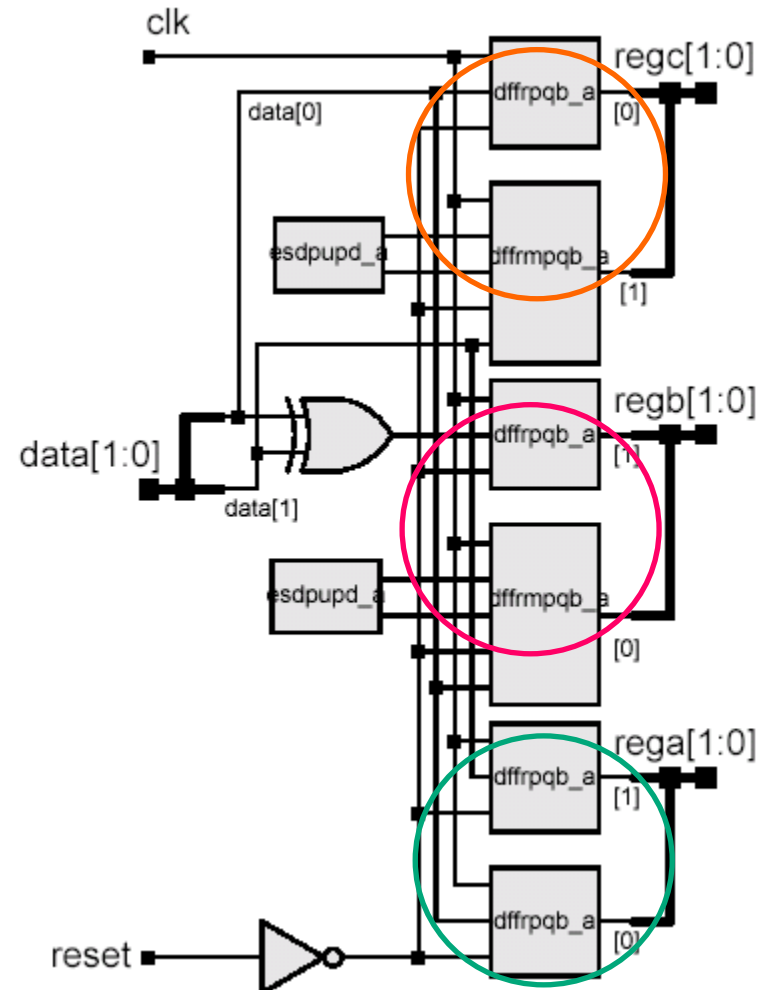Note: regc gets the new value of regb in the same clock cycle.




Synthesis of Multi-Cycle Operations
 
```
module m_cycle (result, data_a, data_b, data_c, clk);  
  input  [3:0] data_a, data_b, data_c;  
  input          clk;  
  output [4:0] result;  
  reg  [4:0] result, temp1;  
  
  always @ ( posedge clk)  
  begin  
    temp1 = data_a + data_b;  
  
    @ (posedge clk)  
    result = temp1 + data_c;  
  end  
endmodule
```



An operation that cannot complete in one cycle must be distributed over multiple clock cycles, i.e. pipelined,


Synthesis Result

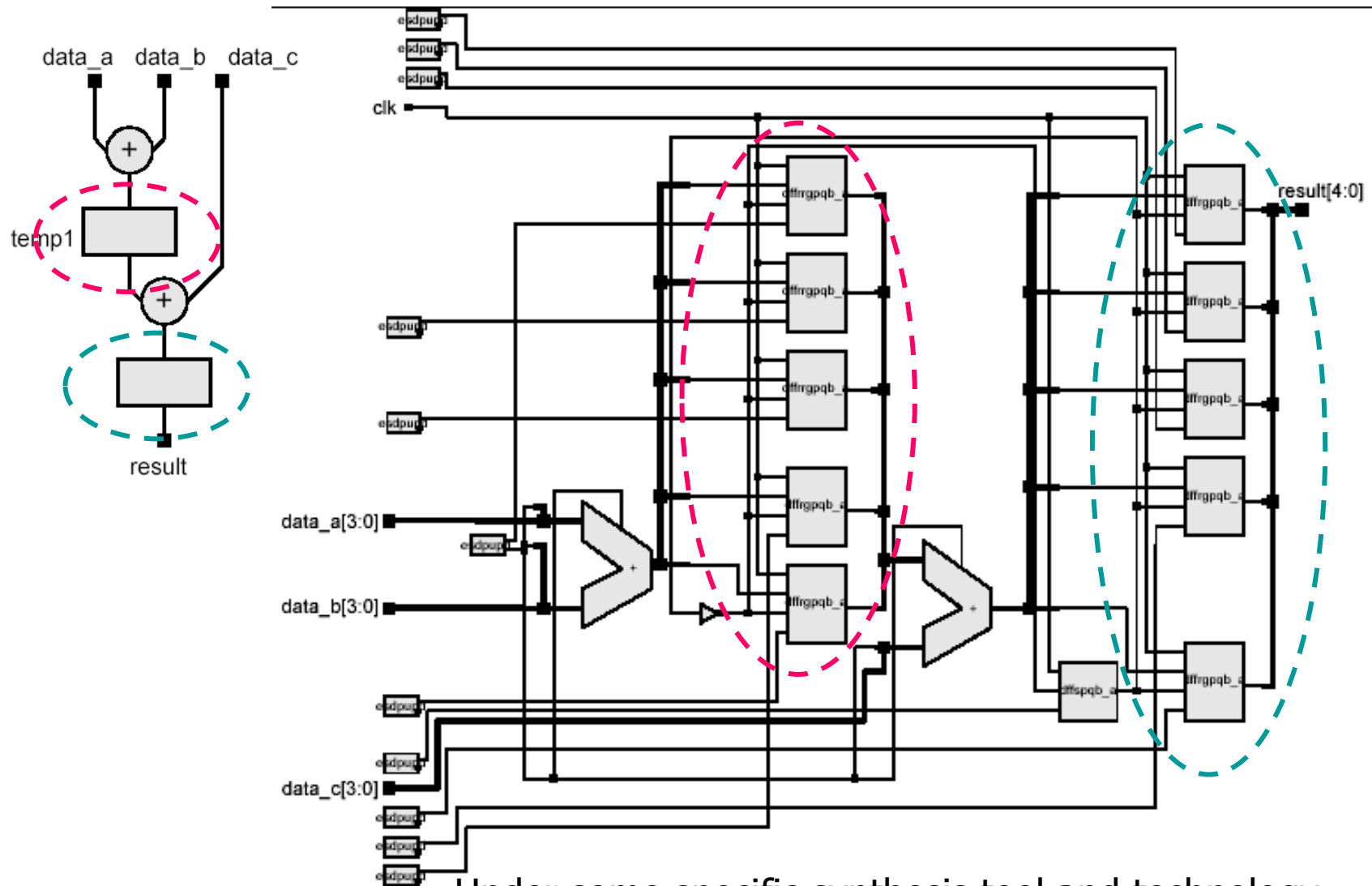


Under some specific synthesis tool and technology

Storage Elements

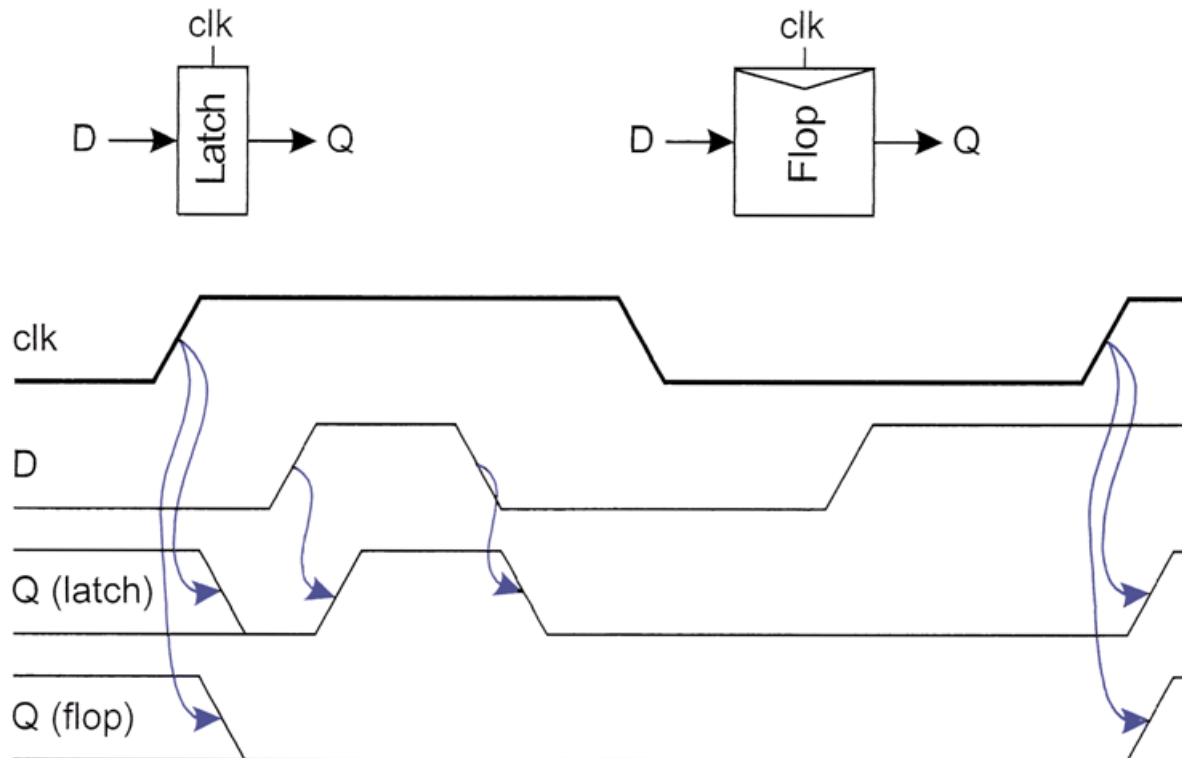- **Latch**: level-sensitive
- **Flip-flop**: edge-triggered
 - D-type, T-type, SR-type, and JK-type.







Flip-Flops

 

Timing Notation


- tpd: logic propagation delay
- tcd: logic contamination delay
- tpcq: flop clock-to-Q propagation delay
- tccq: flop clock-to-Q contamination delay
- tsetup: flop setup time
- thold: flop hold time

Timing Diagrams

    

Max-Delay Constraint of Flip-Flops (1/2)
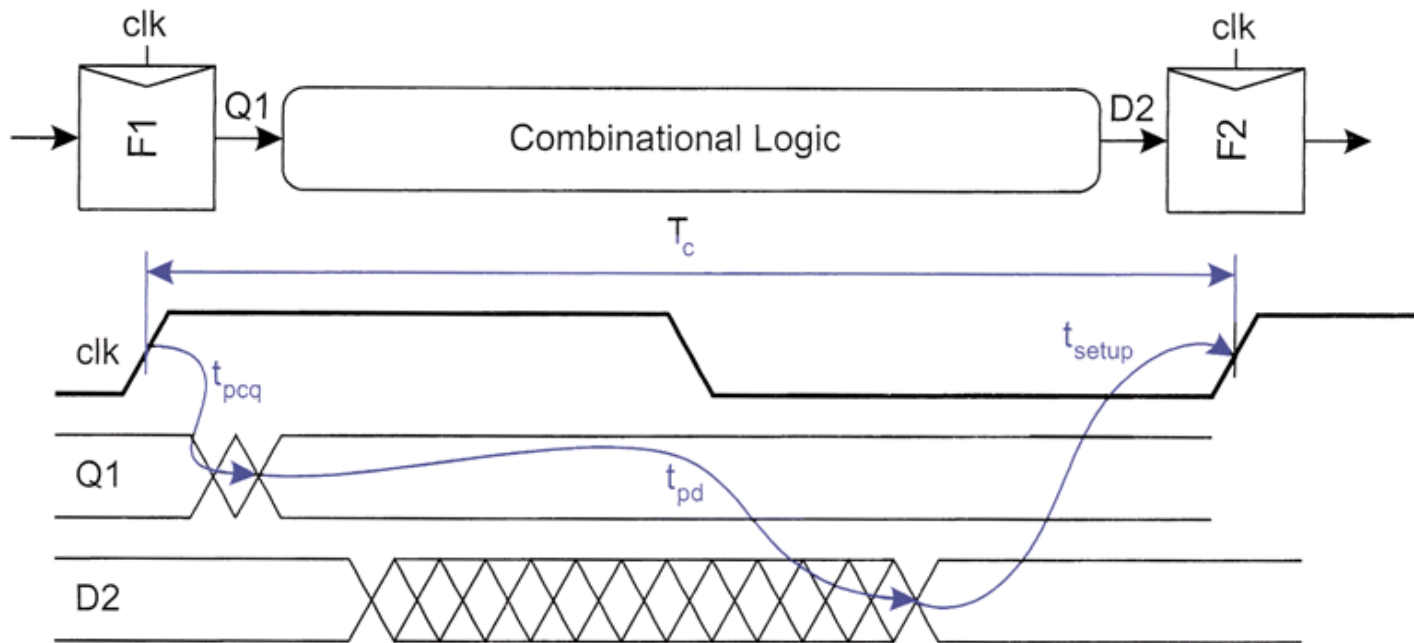
$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$



Max-Delay Constraint of Flip-Flops (2/2)

■ Setup time failure (max-delay failure)


- If the combinational logic delay is too long, the receiving element will miss its setup time and sample the wrong value.

■ Solution


- Redesign the logic to be faster.
- Increase the clock period.

$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

Min-Delay Constraint of Flip-Flops (1/2)

 
 
$$t_{ccq} + t_{cd} \geq t_{\text{hold}}$$



Min-Delay Constraint of Flip-Flops (2/2)


- Hold time failure (min-delay failure, race condition)
 - If the hold time is large and the contamination delay is small, data can incorrectly propagate through two successive elements on one clock edge, corrupting the system state.
- Solution
 - Redesign the logic to be slower.

$$t_{ccq} + t_{cd} \geq t_{\text{hold}}$$

Collapsing of Nets

An internal net declared in the source description may be eliminated by the optimization process.
 
```
module and_gate(y, a, b, c);  
  input    a, b, c;  
  output   y;  
  wire     y1, y2;  
  
  assign y1 = a & b;  
  assign y2 = c & b;  
  assign y  = y1 & y2;  
endmodule
```




A net that is declared as a primary input or output will be retained in the synthesized design.

Elimination of Register Variables

A register variable declared in the source description may be eliminated by the optimization process.
 
```
module n_gate1 (y, gate_in);  
  parameter      size = 3;  
  input [size-1:0] gate_in;  
  output         y;  
  reg            y_int;  
  integer        k;    // Loop control  
  assign y = y_int;
```



```
always @ (gate_in)  
  begin : look_for_0  
    y_int = 0;  
    for (k=0; k <= size-1; k=k+1)  
      if (gate_in[k] == 0) begin  
        y_int = 1;  
        disable look_for_0;  
      end  
    end  
  end  
endmodule
```

Note: Both *k* and *y_int* are eliminated.

The same result is obtained if *reg [size-1:0] k* is declared for the loop control.

Memory Synthesis


```
module sn54170 (data_in, wr_sel, rd_sel, wr_enb, rd_enb, data_out);
  input          wr_enb, rd_enb;
  input          [1:0] wr_sel, rd_sel;
  input          [3:0] data_in;
  output         [3:0] data_out;

  reg            [3:0] latched_data [3:0]; // 4*4 bits

  always @ (wr_enb or wr_sel or data_in) begin
    if (!wr_enb) latched_data[wr_sel] = data_in;
  end // write

  assign data_out = (rd_enb) ? 4'b1111 : latched_data[rd_sel];
                                     // read
endmodule
```

Synthesis Result

 


Synthesis of Arithmetic Operators (1/2)

assign quotient [7:0]=dividend [7:0] / 8;

EXAMPLE

1000 >> 3 = 0001

Zeros automatically fill from behind.

 

Division by a power of 2 will be recognized as a right-shift and synthesized as a re-wired bus, without gates.

Synthesis of Arithmetic Operators (2/2)


REMAINDER (%) WILL BE IMPLEMENTED AS A PART-SELECT IF THE DIVISOR IS A POWER OF 2.

EXAMPLE: $100\boxed{1}_2 \% 0010_2 = 0001_2$ All but the LSB are divisible by 2.


EXAMPLE: $10\boxed{10}_2 \% 0100_2 = 0010_2$ The bits to the left of 2^2 are divisible by 2^2 .

PART-SELECT DOES NOT REQUIRE GATES.

Synthesis of Relational Operators (1/2)

 

 The difference $A - B$ in a sign-extended format reveals the relative magnitude of A and B in finite word length arithmetic. $A > B$ if the **extended bit** is 0.



Synthesis of Relational Operators (2/2)


```
module relational_identity_4bit
  (A_eq_B, A_noteq_B, A_gt_B, A_gteq_B, A_lt_B, A_lteq_B, A, B);
  output      A_eq_B, A_noteq_B, A_gt_B, A_gteq_B, A_lt_B, A_lteq_B;
  input      [3:0] A, B;

  assign A_eq_B = (A == B);
  assign A_noteq_B = (A != B);
  assign A_gt_B = (A > B);
  assign A_gteq_B = (A >= B);
  assign A_lt_B = (A < B);
  assign A_lteq_B = (A <= B);

endmodule
```

Note shared logic in synthesis result.

Synthesis Result

 

Synthesis of Equality Operators

```
module identity_4bit (A_eq_B, A_noteq_B, A, B);
```


```
    output      A_eq_B, A_noteq_B;
```

```
    input  [3:0] A, B;
```

```
    assign A_eq_B = (A == B);
```

```
    assign A_noteq_B = (A != B);
```

```
endmodule
```

 


Synthesis of Reduction Operators (1/2)

```
module reduction
  (data_word, y_red_and, y_red_or, y_red_nand, y_red_nor, y_red_xor, y_red_xnor);
  input   [1:0] data_word;
  output   y_red_and, y_red_or, y_red_nand,
           y_red_nor, y_red_xor, y_red_xnor;
  reg      y_red_and, y_red_or, y_red_nand,
           y_red_nor, y_red_xor, y_red_xnor;

  always @ (data_word) begin
    y_red_and  <= &    data_word;
    y_red_or   <= |    data_word;
    y_red_nand <= ~&   data_word;
    y_red_nor  <= ~|   data_word;
    y_red_xor  <= ^    data_word;
    y_red_xnor <= ~^   data_word;
  end
endmodule
```

Synthesis of Reduction Operators (2/2)

 

Synthesis of Bitwise Operators (1/2)

```
module bitwise (  
    data_a, data_b, data_c, data_d, data_e, data_f, data_g, data_h,  
    data_i, data_j, data_k, data_l, data_m,  
    y_bit_and, y_bit_or, y_bit_nand,  
    y_bit_nor, y_bit_xor, y_bit_xnor, y_bit_neg);  
  
    input      [1:0] data_a, data_b, data_c, data_d, data_e, data_f, data_g  
                  data_h, data_i, data_j, data_k, data_l, data_m;  
    output [1:0] y_bit_and, y_bit_or, y_bit_nand, y_bit_nor,  
                  y_bit_xor, y_bit_xnor, y_bit_neg;  
    reg      [1:0] y_bit_and, y_bit_or, y_bit_nand, y_bit_nor,  
                  y_bit_xor, y_bit_xnor, y_bit_neg;
```

Synthesis of Bitwise Operators (2/2)

```

always @ (data_a or data_b or data_c or data_d or data_e or data_f or
          data_g or data_h or data_i or data_j or data_k or data_l or data_m)

```

begin

```

y_bit_and  = data_a & data_b;
y_bit_or   = data_c | data_d;
y_band     = data_e & data_f;
y_bit_nand = ~y_band;
y_bor      = data_g | data_h;
y_bit_nor  = ~y_bor;

y_bit_xor  = data_i ^ data_j;
y_bit_xnor = data_k ~^ data_l;
y_bit_neg  = ~data_m;


```

or

```

end
endmodule

```

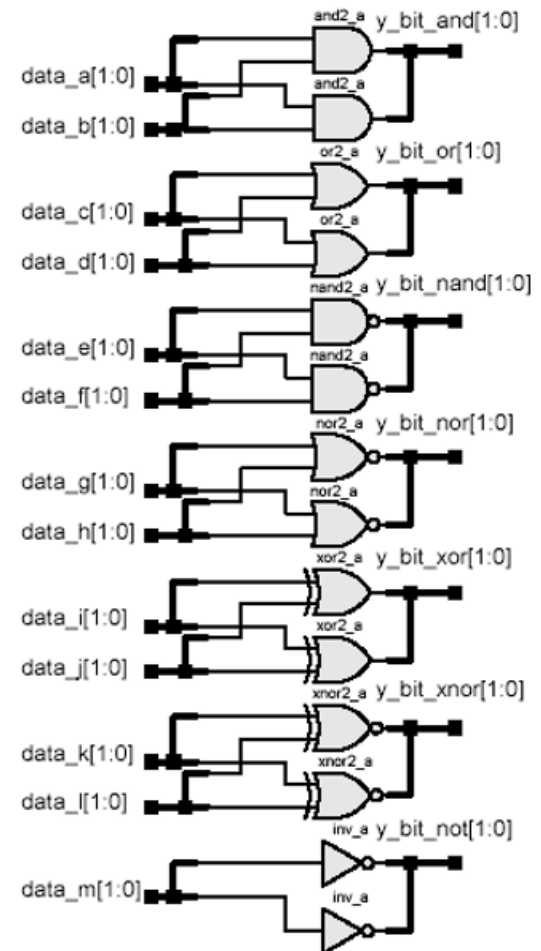

Synthesis of Conditional Operator (1/2)

```
module equality_if_4bit (data_out, data_a, data_b, data_c, data_d, sel);
  input [3:0]    data_a, data_b, data_c, data_d;
  input [1:0]    sel;
  output        data_out;
  reg           data_out;

  always @ (data_a or data_b or data_c or data_d or sel)
    begin
      if (sel == 2'b00) data_out = data_a; else
      if (sel == 2'b01) data_out = data_b; else
      if (sel == 2'b10) data_out = data_c; else
                          data_out = data_d;           // For illustration
    end
endmodule
```


Synthesis of Conditional Operator (2/2)

```
module mux_conditional (data_out, data_a, data_b, data_c, data_d, sel);  
  input  [3:0] data_a, data_b, data_c, data_d;  
  input  [1:0] sel;  
  output [3:0] data_out;  
  
  assign data_out = (sel == 2'b00) ? data_a :  
                    (sel == 2'b01) ? data_b :  
                    (sel == 2'b10) ? data_c : data_d;  
  
endmodule
```

The conditional operator synthesizes into library muxes or equivalent gates. A conditional operator with feedback will synthesize into a latch. A conditional operator with an assignment of 'z' will synthesize to a three-state gate.


Synthesis Result (1/2)

 Synthesis in library having only a two-channel mux:





Synthesis Result (2/2)

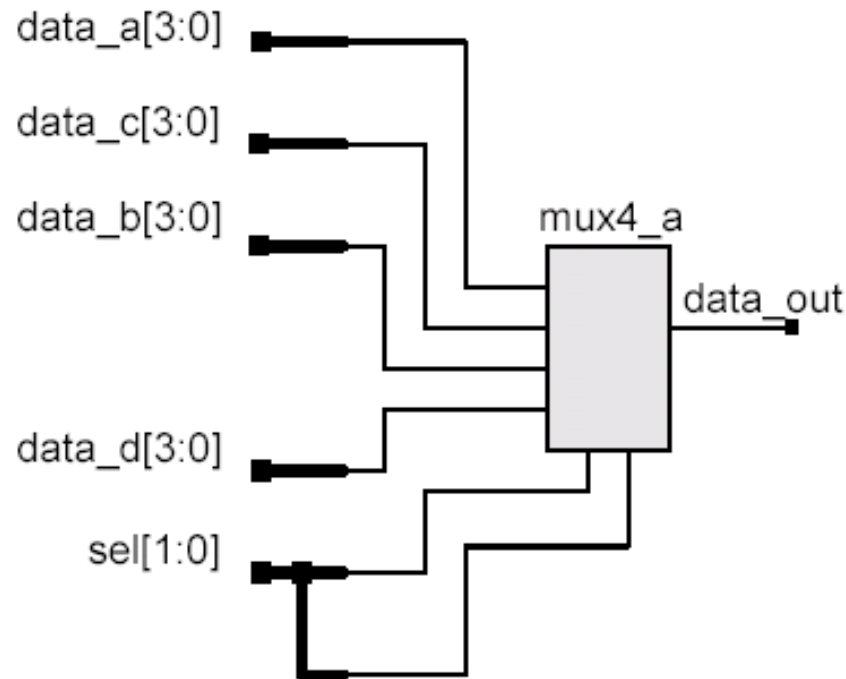Synthesis in a library having a four-channel mux:



Grouping of Operators
  
```
module operator_group  
  (sum1, sum2, a, b, c, d);  
  input    [3:0] a, b, c, d;  
  output   [4:0] sum1, sum2;  
  
  assign sum1 = a + b + c + d;  
  assign sum2 = (a + b) + (c + d);  
  
endmodule
```



Synthesis of “case” Statements (1/2)

```

module alu_reg_with_z1 (alu_out, en, a, b, s0, s1, s2, clk, reset);
  output      [1:0] alu_out;
  input       [1:0] a, b;
  input       en, s0, s1, s2, clk, reset;
  reg        [1:0] out_int;

```

```

  assign alu_out = (en == 1) ? out_int : 2'bz;

```

```

  always @ (posedge clk)

```

```

    if (reset) out_int = 2'b0;

```

```

    else

```

```

      case ({s0,s1,s2})

```

```

        3'b111 : out_int = a & b;

```

```

        3'b011 : out_int = a | b;

```

```

        3'b001 : out_int = a ^ b;

```

```

        default: out_int = 2'bx;

```

```



      endcase

```

```

    endmodule

```

  


Synthesis of “case” Statements (2/2)

```
module alu_reg_with_z2 (alu_out, data_a, data_b, enable, opcode, clk, reset);  
  input      [2:0] opcode;  
  input      [3:0] data_a, data_b;  
  input      enable, clk, reset;  
  output [3:0] alu_out;  
  reg [3:0] alu_reg;
```

```
  assign alu_out = (enable == 1) ? alu_reg : 4'bz;
```

```
  always @ (posedge clk)  
    if (reset) alu_reg = 0; else  
      case (opcode)  
        3'b001: alu_reg = data_a | data_b;  
        3'b010: alu_reg = data_a ^ data_b;  
        3'b101: alu_reg = data_a & data_b;  
        3'b110: alu_reg = ~data_b;  
        default: alu_reg = 0;
```
 
```
      endcase  
    endmodule  
    // Less flexibility
```



Reference

1. 教師自製
2. Modeling, Synthesis, and Rapid Prototyping with the Verilog HDL, Michael D. Ciletti, ISBN: 0139773983, Prentice Hall, 1999.

